

## **GATE ESE 2020 TARGET ECE ENGINEERING**

## **GATE ESE PSU's 2019-20**

## **GATEACADEMY**

### **101 ANALOG SYSTEM\_GATEACADEMY**

**TOTAL PAGE ANALOG SYSTEM-754 PGAE**

### **LATEST GATEACADEMY CLASSROOM HANDWRITTING**

#### **CONTENT COVERED:**

- 1. Theory Notes**
- 2. Explanation**
- 3. Derivation**
- 4. Example**
- 5. Shortcut & Formula Summary**
- 6. Previous year Paper Q. Sol.**


**Noted:- Single Source Follow, Revise**

**Multiple Time Best key of Success**

## Diode Circuits
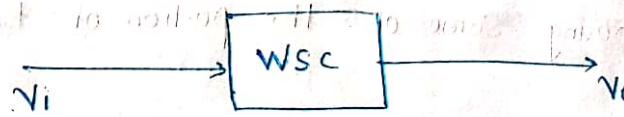
### \* Wave shaping Circuits

of basic waveforms obtained from simple supply  
differentiation and integration process is called as wave shaping









- It is used for changing the shape of waveforms.
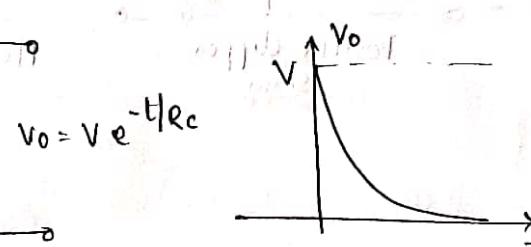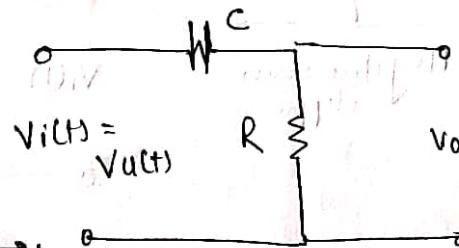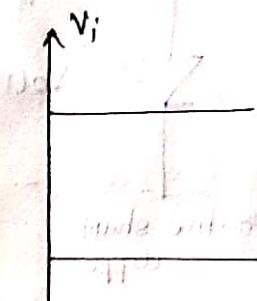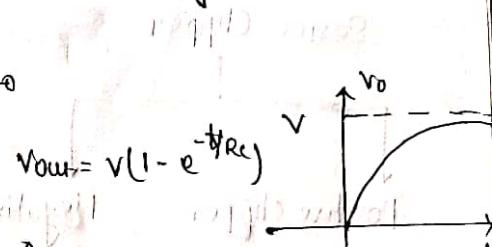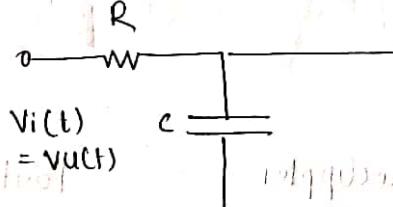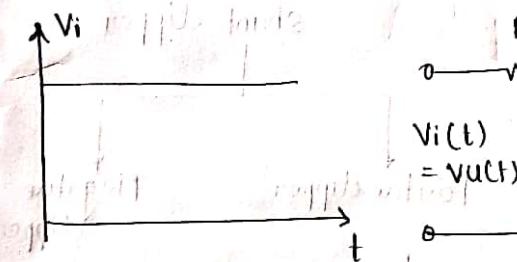
### WSC


Linear WSC  
based on linear element  
 $R, L, C$   
eg: RC HPF LPF

Non-linear WSC  
Based on Nonlinear element  
like diode  
eg Half wave Rectifier



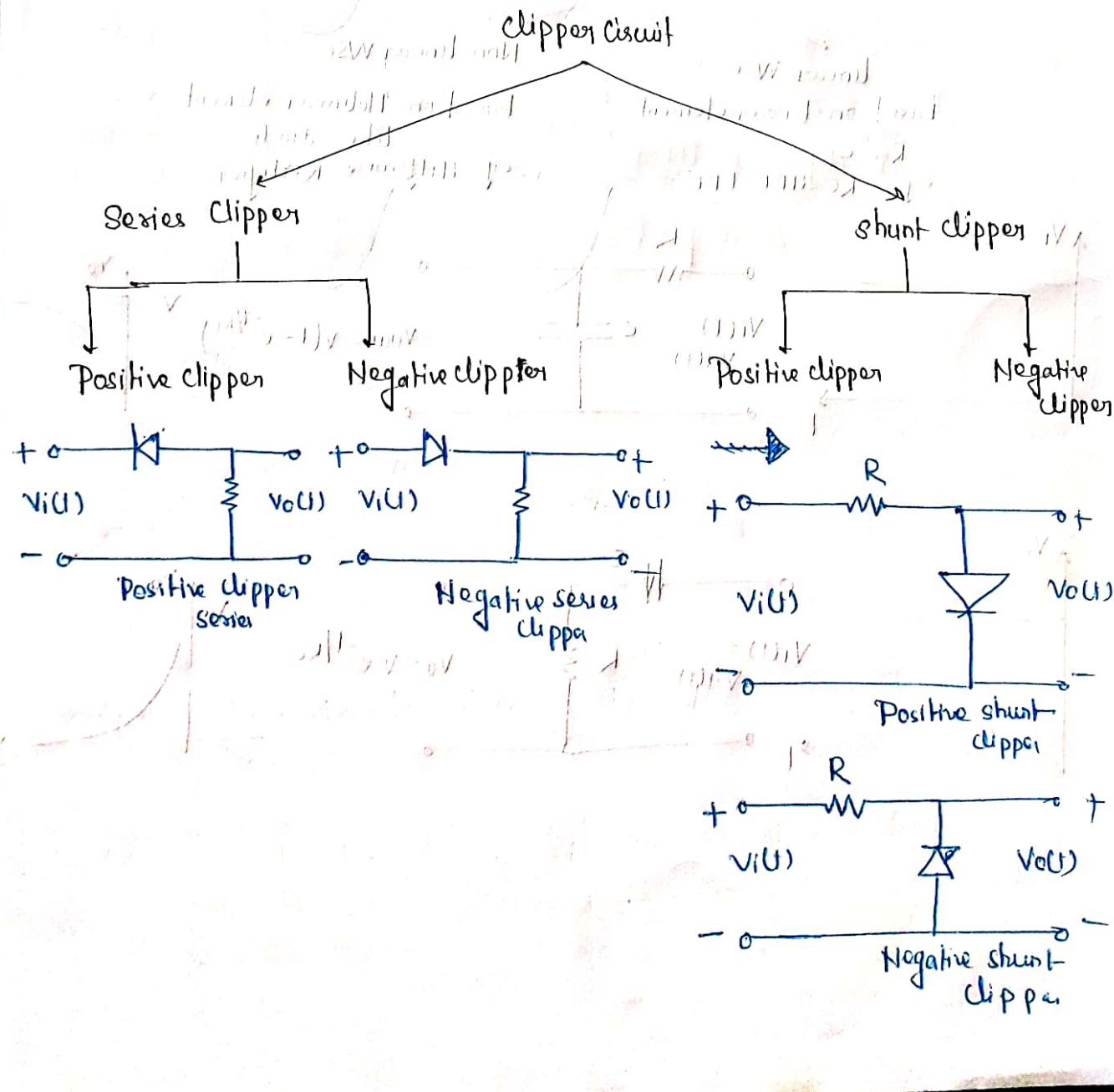
## \* Clipper Circuits



- Clipper Circuit is a non linear WSC which is used for clipping or removing some of the portion of transmitted waveform.
- The Main Circuit element is diode
- Clipper circuit is also referred as amplitude limiter or amplitude selector circuit.
- Classification of clipper circuit



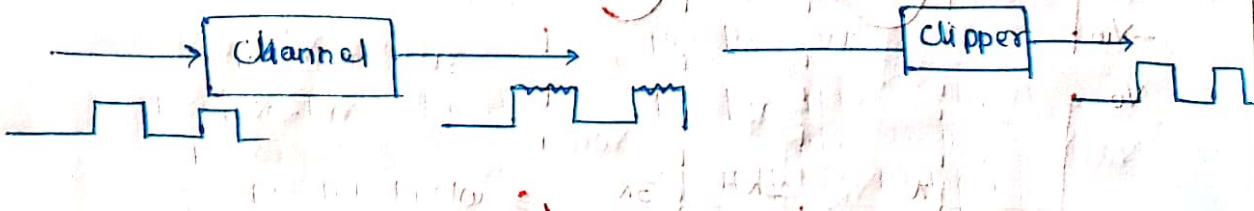
- In Series clipper Circuit diode is connected in series and in shunt clipper circuit diode is connected in parallel (structure wise)
- Positive clipper circuit removes maximum portion of x mitted wave form.
- Negative clipper circuit removes maximum portion of x mitted wave form.
- clipper circuit can be used for eliminating the effect of noise from waveform in digital communication.




### \* Positive Series Clipper Circuit

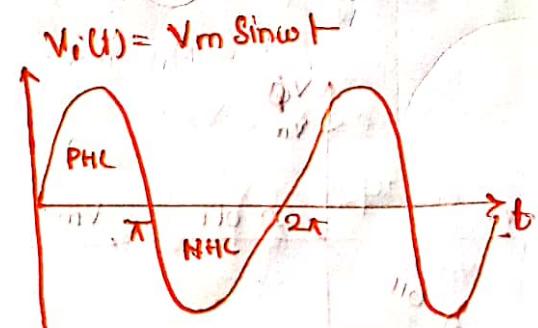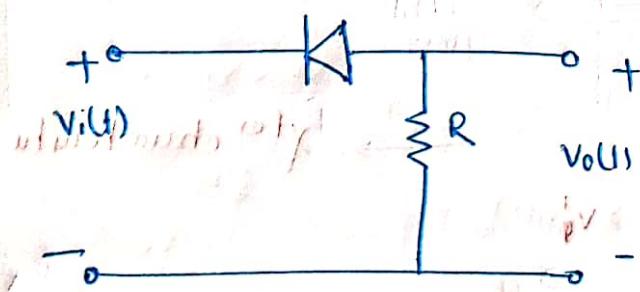

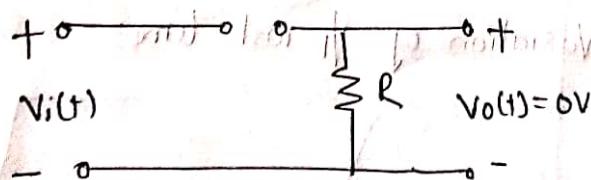- During positive half cycle (PHC) ( $0 < \omega t < \pi$ )  
Diode = Reverse Bias (RB)




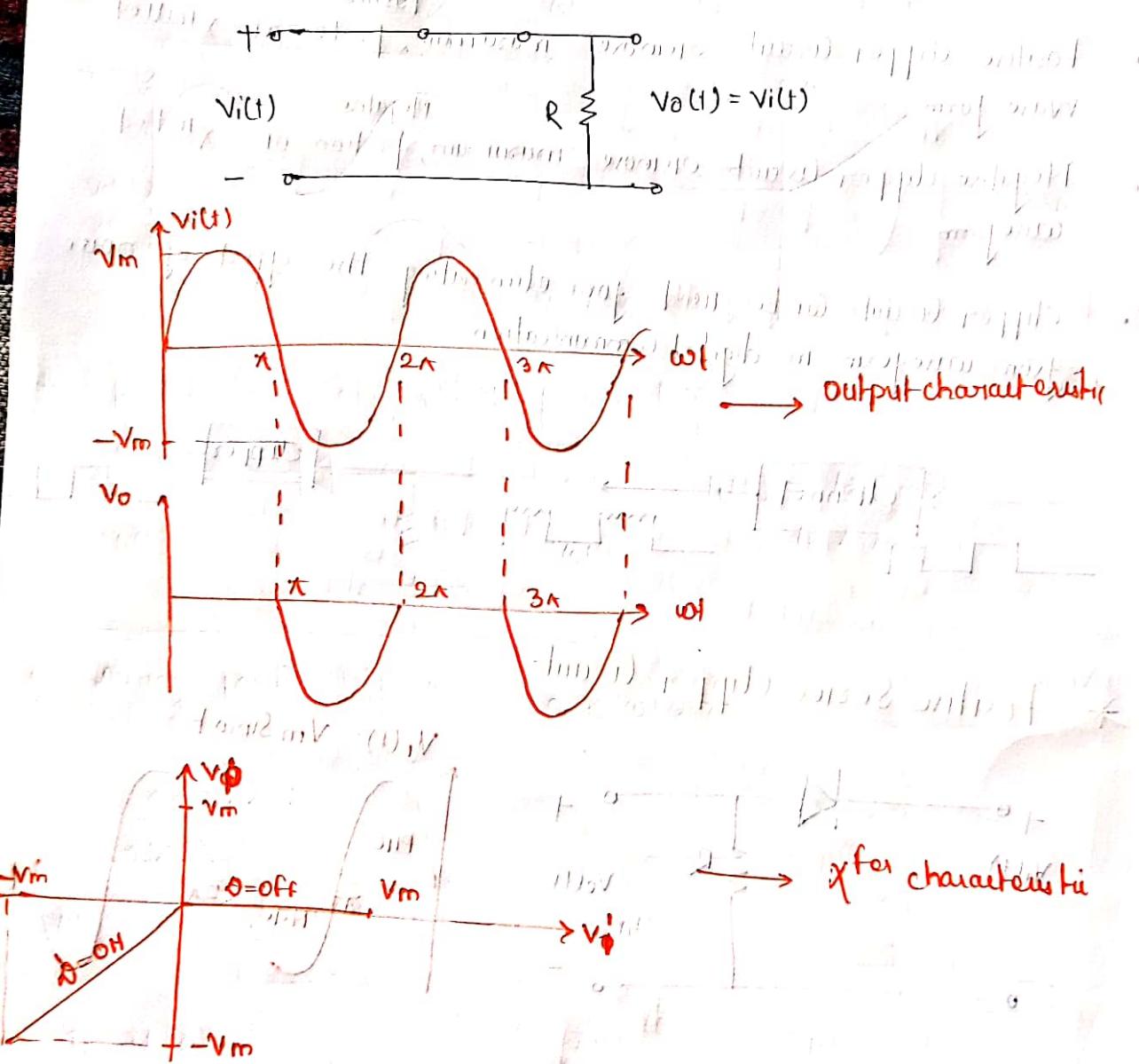- During Negative Half cycle Diode = forward biased (FB)  $\pi < \omega t < 2\pi$




- output characteristic describe the variation of o/p wrt time
- $\chi_{\text{for}} \text{ characteristic}$  describe variation of i/p wrt time

\* Negative Series clipper

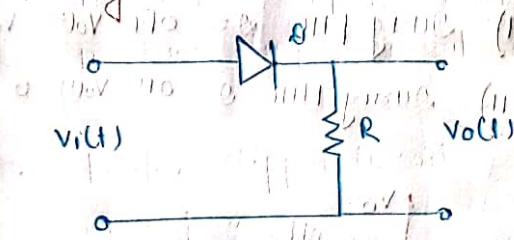


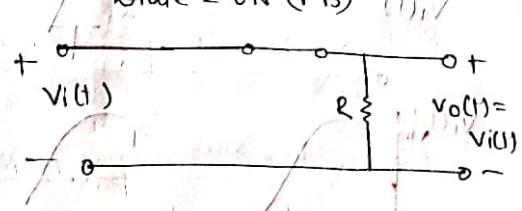i) During positive half cycle  $0 < \omega t < \pi$   
State = ON (FB)




ii) During Negative half cycle  $\pi < \omega t < 2\pi$

D = OFF

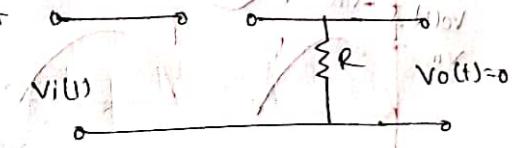


$V_{i(t)}$

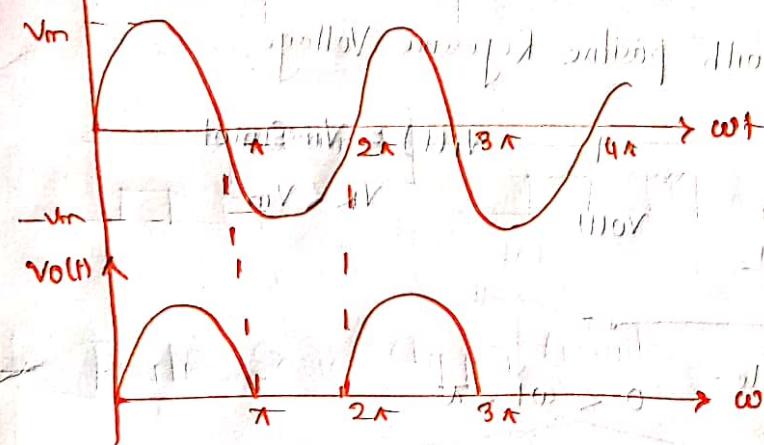

Output charac.

\* Positive shunt clipper circuit

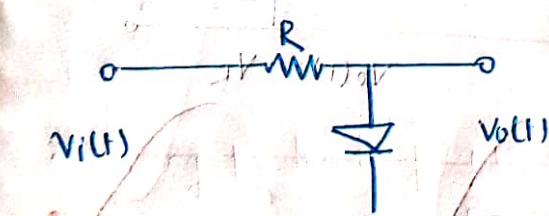

i) PHC


D → ON

$$V_o(t) = \cancel{V_i(t)} 0$$


ii) NHC

(D → off)

$$V_o(t) = V_i(t)$$

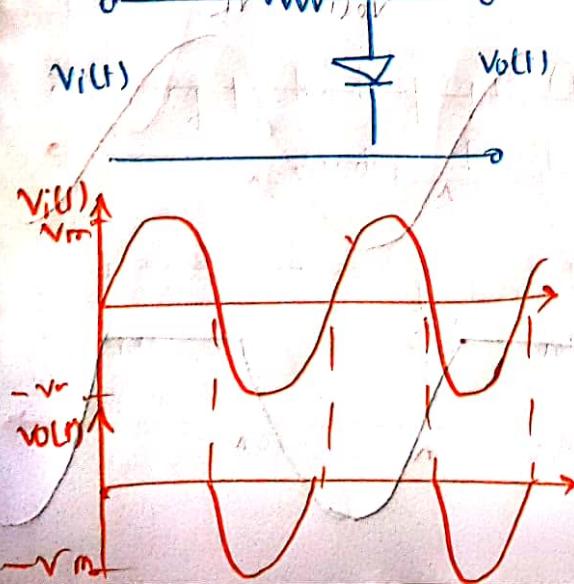


### \* Negative shunt clipper circuit

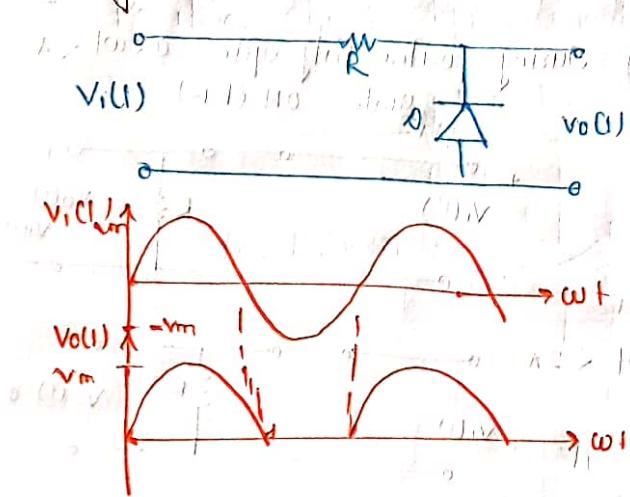


i) During PHC,  $\theta = \text{OFF}$   $V_{o(t)} = V_i(t)$



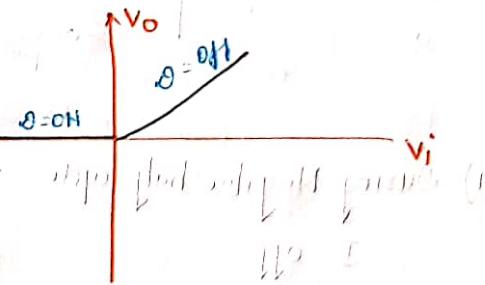
ii) During NHC,  $\theta = \text{ON}$   $V_{o(t)} = 0$


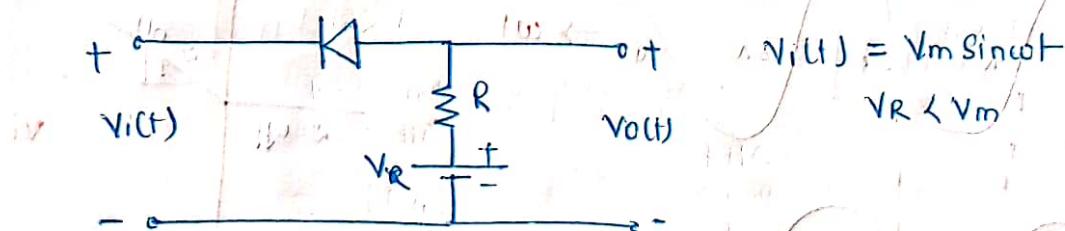
### \* Positive Series clipper with positive Reference Voltage



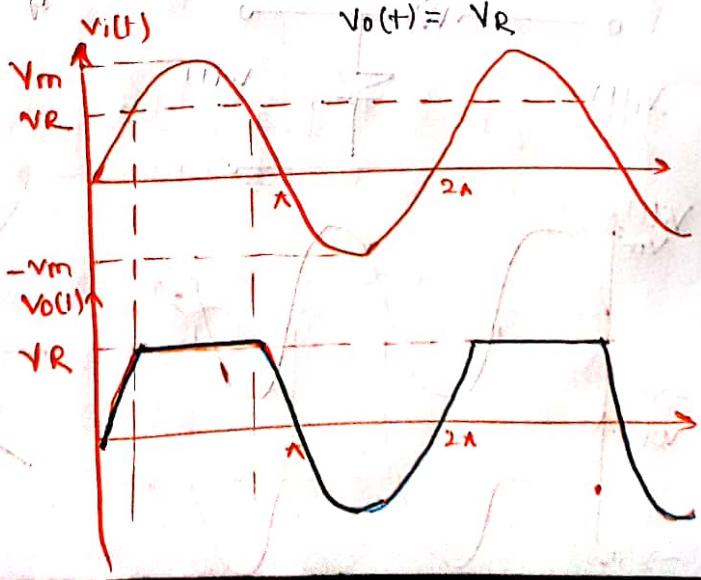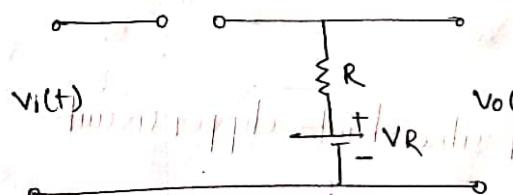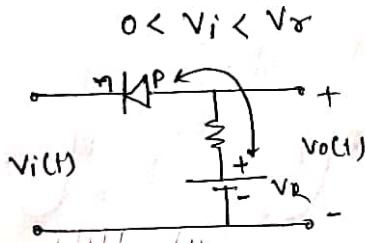i) During positive Half cycle  $0 < \omega t < \pi$



$$ID = f(VR)$$

$$\theta = \text{ON}$$


$$-Vi + 0 + I_\theta R + VR = 0$$

$$I_\theta = \frac{Vi - VR}{R}$$

$$V_o = I_\theta R + VR = Vi$$

2) During Negative half Cycle :


$$\pi < \omega t < 2\pi$$

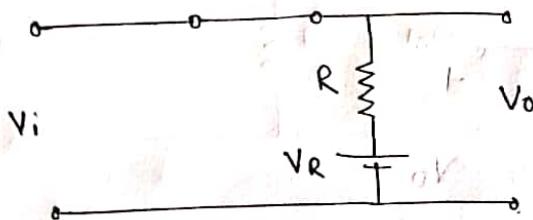


$$\theta = f(V_i) \text{ or } \theta = f(V_R)$$

$$V_o(t) = V_i(t)$$

$$I_{max} V = IV$$

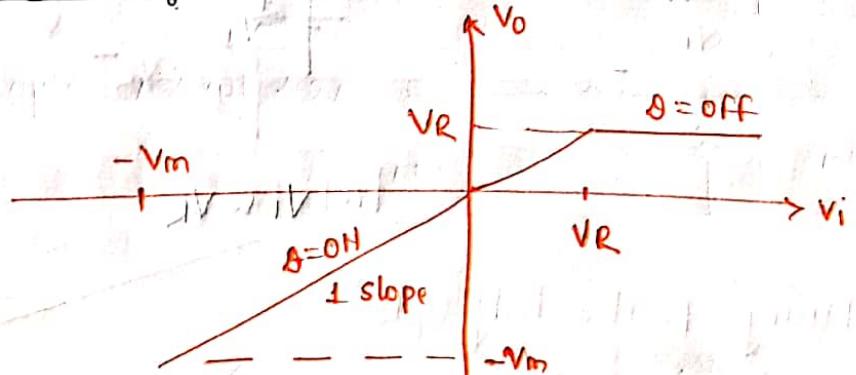

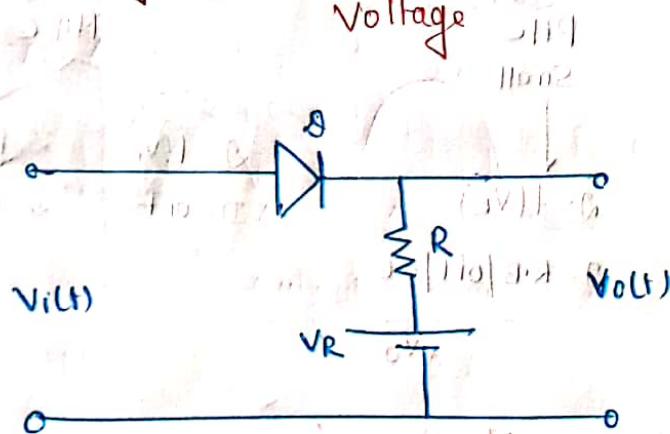\* Negative Series clipper Circuit with Positive Reference Voltage





$$V_R < V_m$$

i)  $V_i > V_R$   
 $\theta = f(V_i) \rightarrow \theta \rightarrow ON$   
 $V_o = V_i$

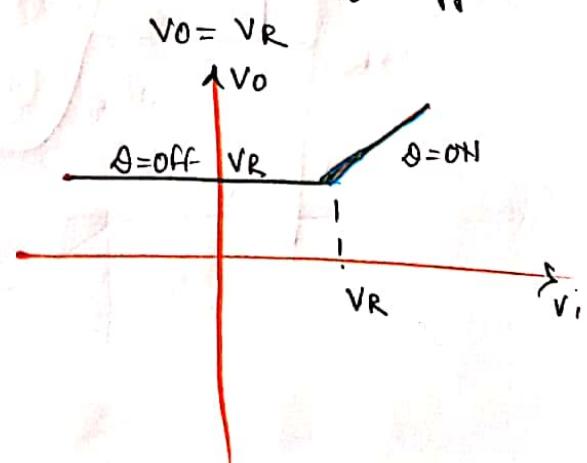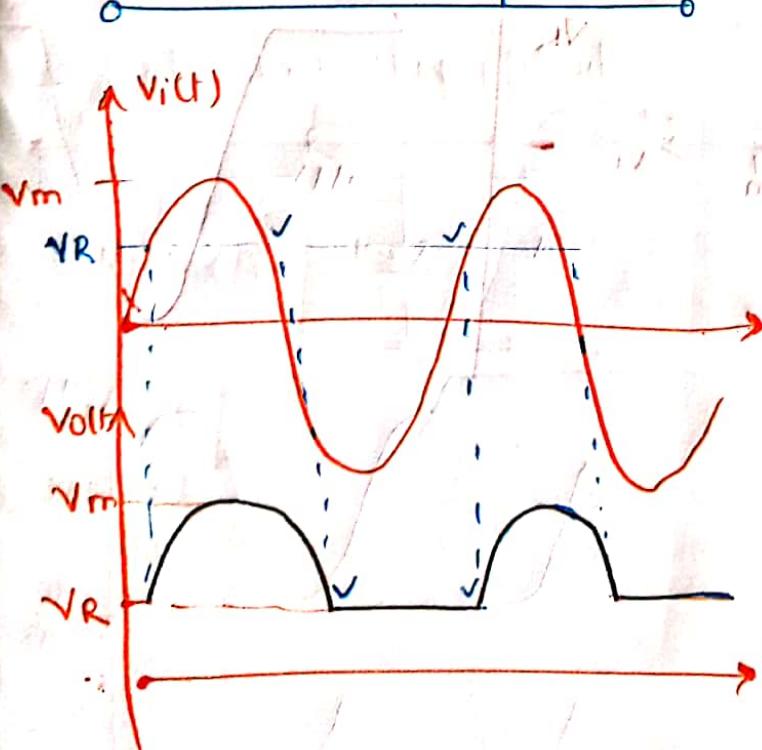
ii)  $V_i < V_R$

PMC  
 $\theta \rightarrow f(V_R)$   
 $\theta \rightarrow OFF$

NHC  
 $\theta \rightarrow f(V_i)$   
 $\text{or}$   
 $\theta \rightarrow f(V_R)$   
 $\theta \rightarrow OFF$


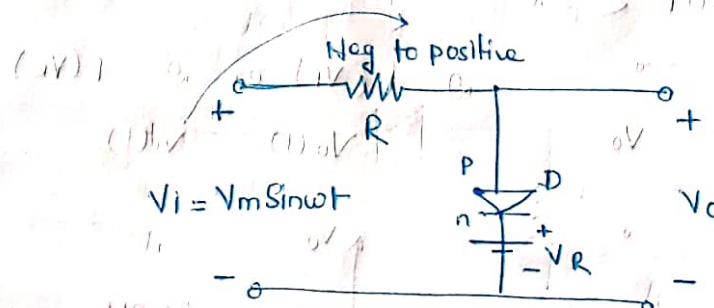
## \* Positive shunt clipper Circuit with Positive Reference Voltage



$V_i & V_R$

During Positive Half Cycle (PHC)

$V_i > V_R$

Positive Half Cycle (PHC)

$$D = f(V_i) \quad \text{on} \rightarrow \text{on}$$

$$D = \frac{V_R}{f_B / \text{sec}}$$

$$V_o = V_R$$

$$V_o = V_R$$

$V_i < V_R$

PHC

Small

$$D = f(V_R)$$

$$D = R \cdot B / \text{off} / \text{on}$$



NH C

$$D = f(V_i)$$


$$D = \text{off}$$

$$D = f(V_R)$$

$$D = \text{off}$$

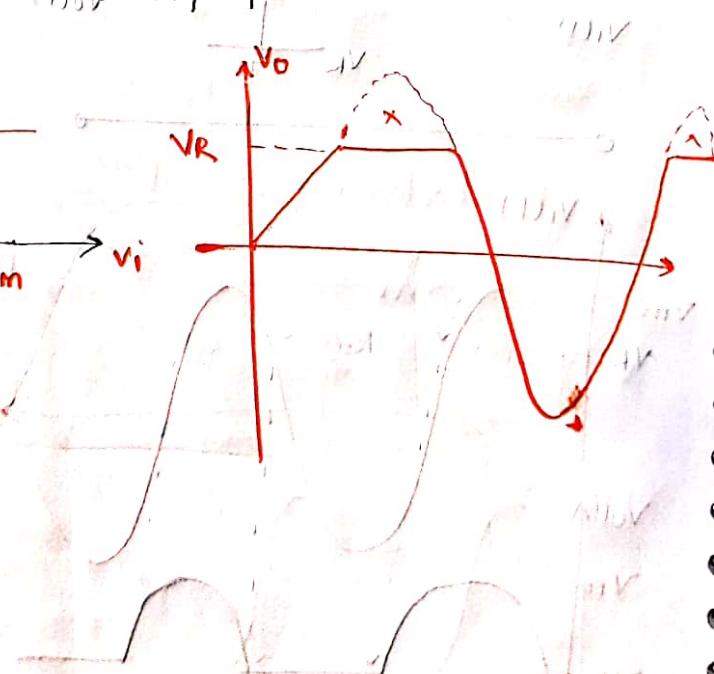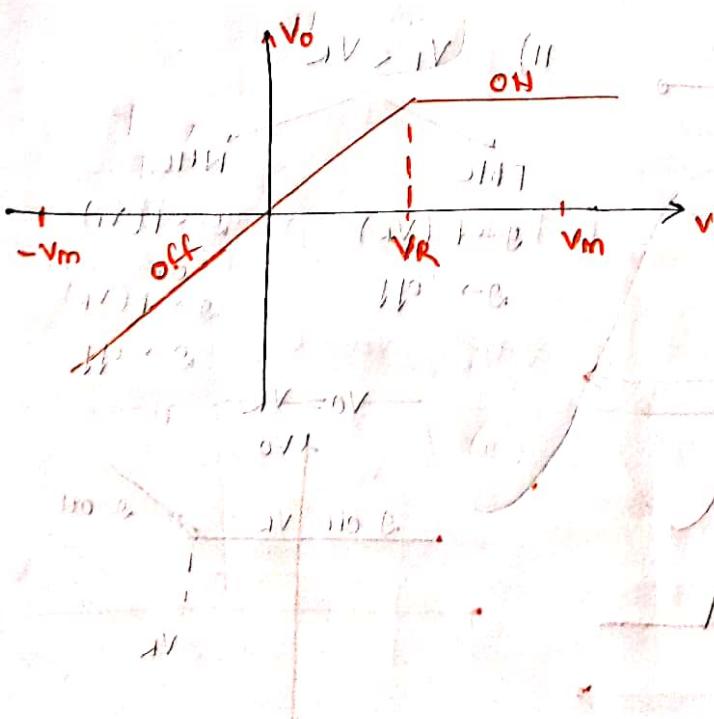

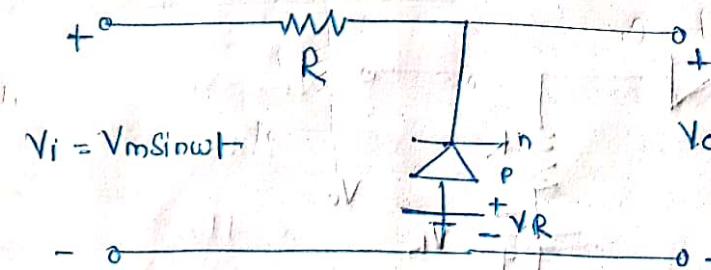\* Negative shunt clipper circuit with positive Ref. Voltage



$$Vi = V_m \sin \omega t$$

$$Vi & VR | \text{inv}, \text{inv}$$

(i) P.H.C. (positive half cycle)

$$Vi > VR$$

P.H.C.

$$\theta = f(V_i)$$

$$\theta = \text{off} / R_B / \text{oc}$$

$$V_o = Vi$$

$$Vi < VR$$

N.H.C.

P.H.C. small

$$\theta = f(V_R)$$

$$\theta = \text{ON} / R_B / \text{sc}$$

$$\theta = f(V_i)$$



$$\theta = \text{ON}$$

N.H.C.

$$\theta = f(V_R)$$

$$\theta = \text{ON}$$

$$No = VR$$

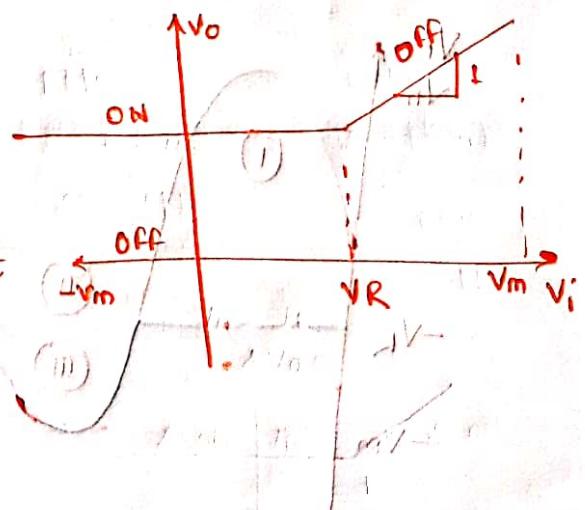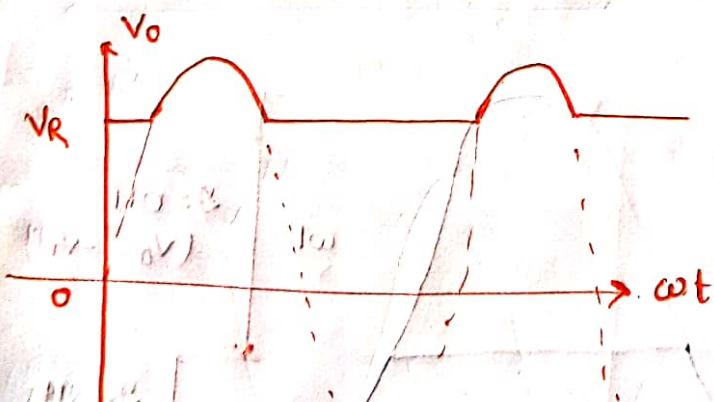

**WANT ECE BEST QUALITY-2019-20**

**LATEST HANDWRITING NOTES**

**BY**

**GATE ACADEMY CLICK HERE**

SAMPLE NOTES WANT FULL NOTES CLICK

***Buy Now***

**Noted-:** Above ECE GATE/IES GATEACADEMY 2019-20

**CLASSROOM BEST QUALITY** Handwriting Notes Unique and Good Handwriting. Above Notes Enough for your Preparation.....


**Noted-:** Dear Aspirants If you do practice previous year paper 50% your work finished.so Guys daily at least 30minutes give previous year.

1. Previous year paper 4-5 times practice before final exam.
2. Subject wise study reference STD book
3. Test series practice more n more (Try to latest test series 2-3 fully solve then join online test series.)

**Noted-: Single Source Follow, Revise**

**Multiple Time Best key of Success**
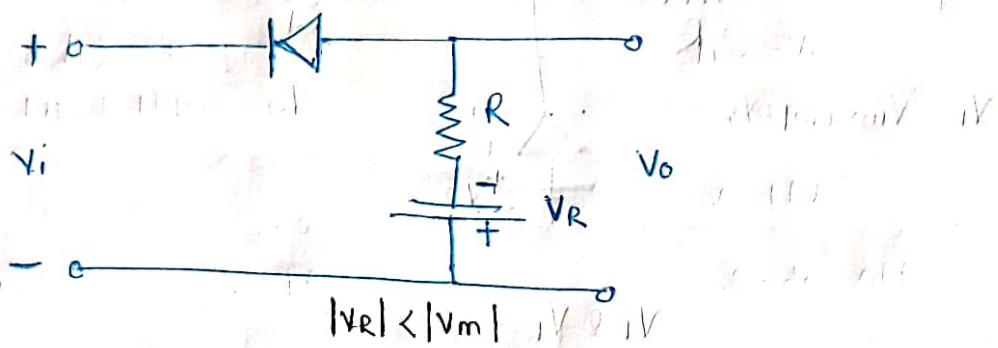
## \* Positive Series Clipper Circuit with negative reference voltage



During positive half cycle

$$\textcircled{I} \quad 0 < \omega t < \pi$$

$$V_i = +ve$$

$$V_R = -ve$$

$$D = f(V_i)$$

$$D = \text{OFF}$$

$$V_o = -V_R$$

During Negative Half Cycle

$$\textcircled{II}$$

$$V_i > -V_R$$

$$D = f(-V_R)$$

$$\text{Diode = OFF}$$


$$\textcircled{III}$$


$$V_i < -V_R$$

$$D = f(V_i)$$

$$\text{Diode = ON}$$

$$V_o = V_i$$

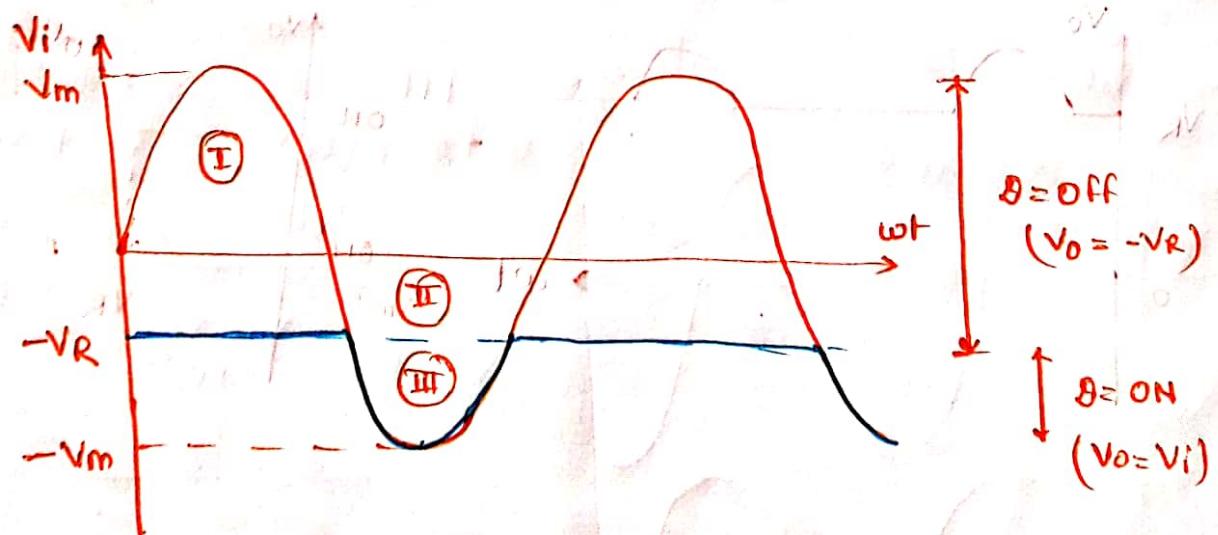

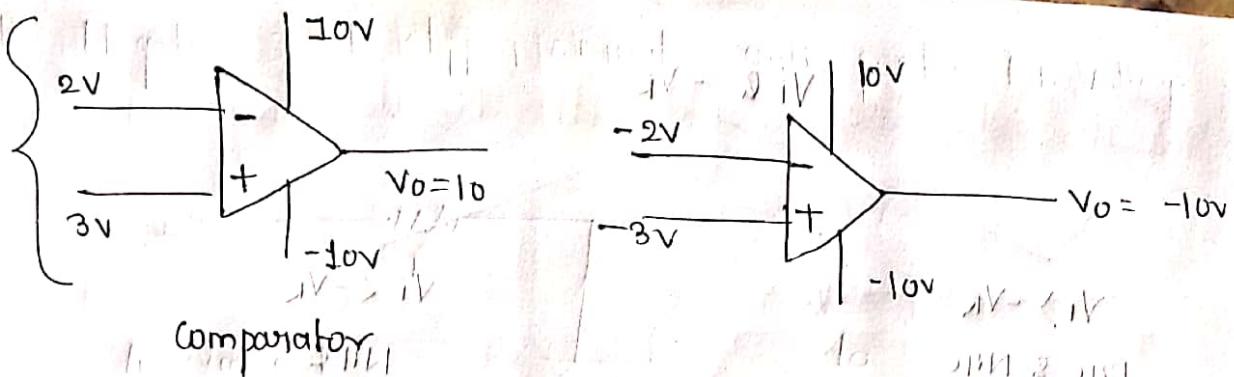


i) non Inverting > Inverting

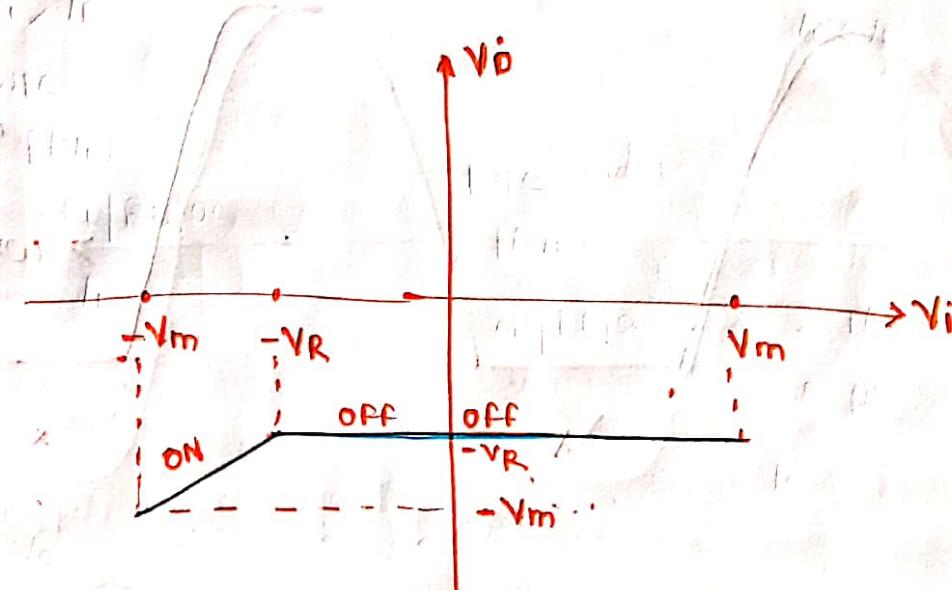
ii) Non Inverting < Inverting

In Comparators, numbers decide the output

In Case of diode, potential decides the output



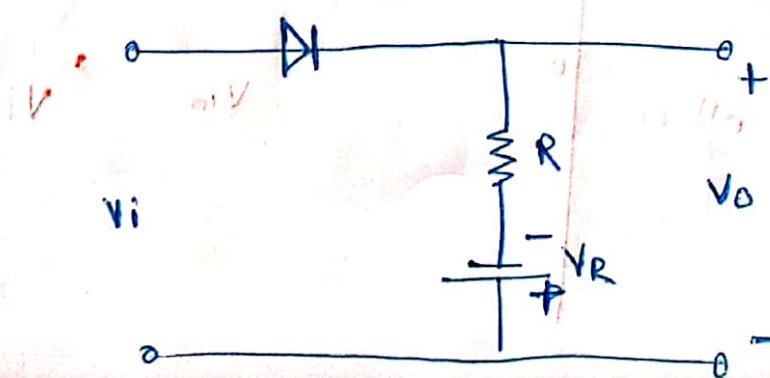\* Negative Series Clipper Circuit with Negative Reference Voltage



## \* Frequency Response of Amplifier \*

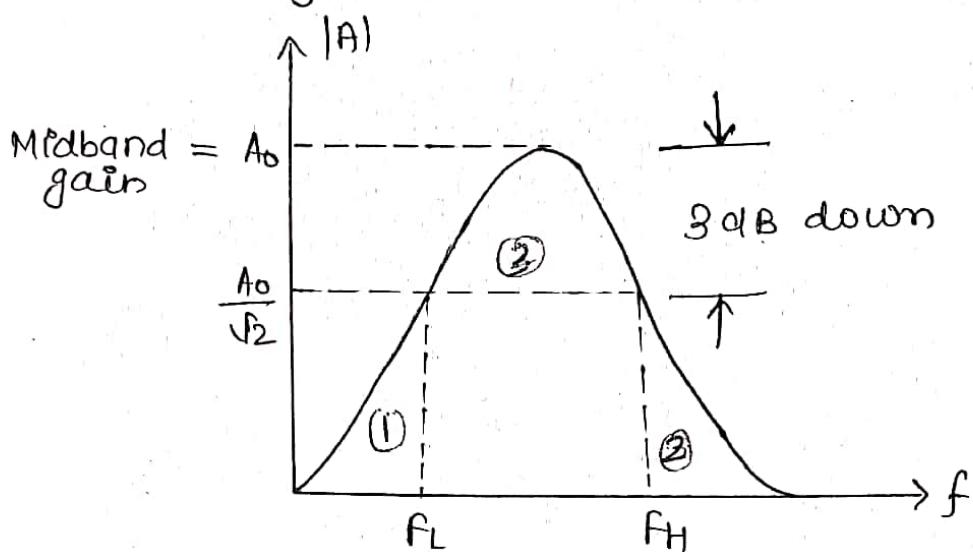


Fig (a). Practical Frequency Response of Amplifier.

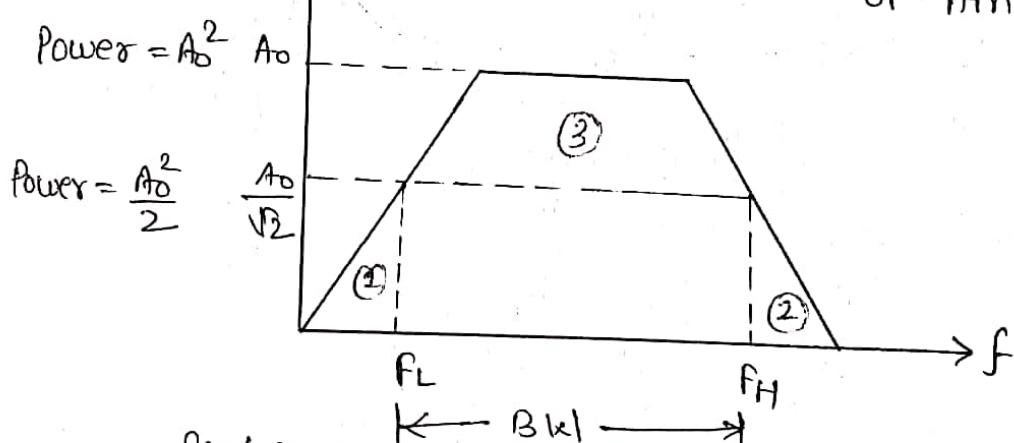


Fig (b) Ideal Frequency Response of Ampr.

\* 3dB Frequency is also known as half power frequency because power gets half at 3dB down.

$$\begin{aligned}
 f_L / f_H &= 3\text{-dB frequency} \\
 &= \text{Half Power frequency} \\
 &= \text{Cut-off frequency} \\
 &= \text{Corner frequency.}
 \end{aligned}$$

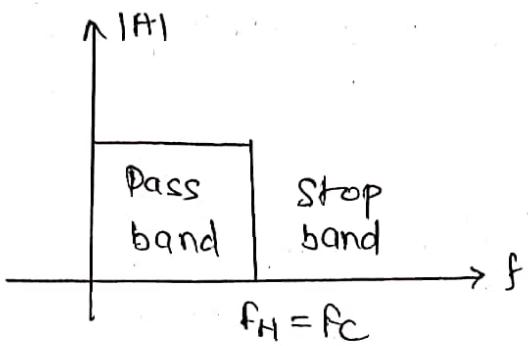


Fig Low pass filter

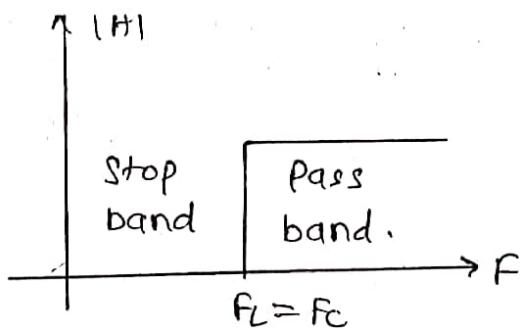


Fig High pass filter

R-1 = low frequency region

R-2 = High frequency region

R-3 = midband frequency flat freq. region.

- \* Low frequency region is described by the characteristics of High Pass Filter.
- \* High frequency region is described by the characteristics of low pass filter.
- \* In both low and high frequency region, gain decreases with frequency.
- \* Midband gain region describes the max. gain of Amp.
- \* BW of Amplifier is given by,  $BW = f_H - f_L$
- \* If  $f_L = 0$  then  $BW = f_H$

example: If 3 dB freq. of Amp is 3MHz then BW will be -

$$BW = 3 \text{ MHz}$$

(If only one 3dB freq. is defined then by default it is upper 3dB freq. i.e.  $f_H$ )

## \* Analysis of higher 3 dB Frequency ( $f_H$ ) -


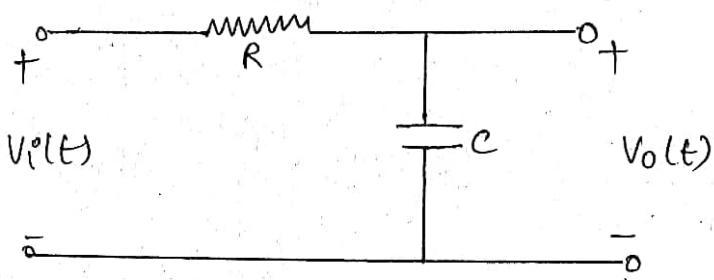


Fig: First order RC Network

(i) Low Frequency Signal (LP)

$$\text{Ideal } (f=0) \quad \therefore X_C = \frac{1}{2\pi f C} = \infty$$


$C \rightarrow 0 \cdot C$

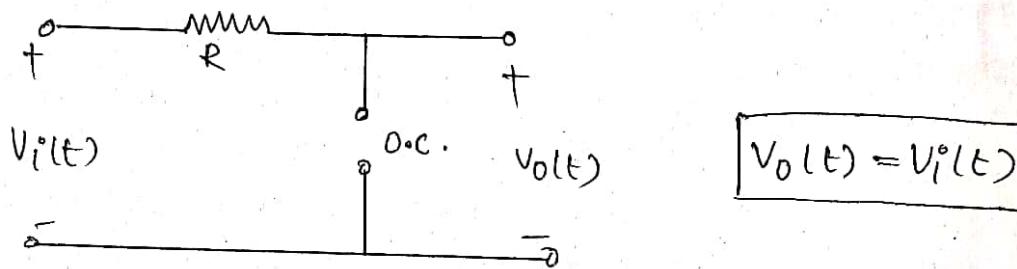

$\therefore$  This nw passes the low freq. signal.

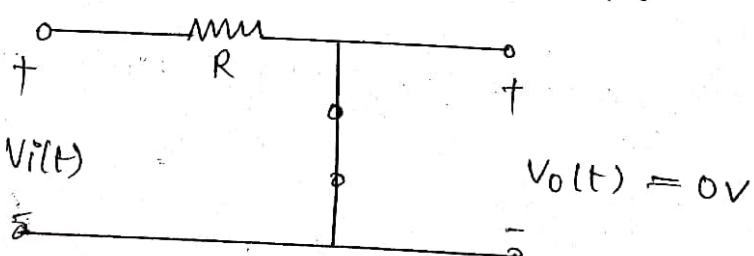(ii) High Frequency Signal (HP)



$$\text{Ideal } (f=\infty) \quad \therefore X_C = \frac{1}{2\pi f C} = 0 \quad \therefore C \rightarrow \infty C$$



$\therefore$  This nw stops the high freq. HP signal.

$\therefore$  The network is a low pass filter circuit  
( LPF :- gives min. attenuation (signal pass) in low freq. and max. attenuation (stops) in high freq. HP signal )— practically

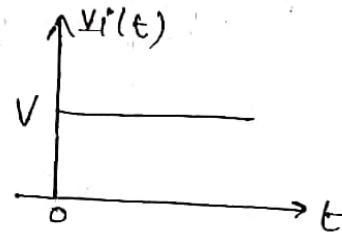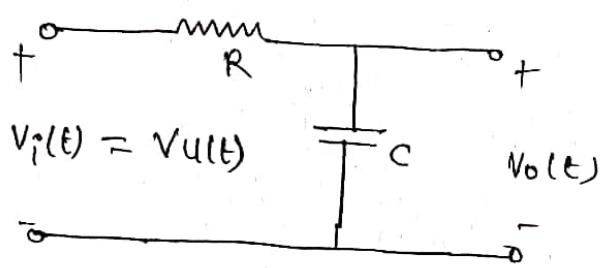\* This RC network is referred as charging circuit or integrator circuit.



$$V_c(t) = V_o(t) = V [1 - e^{-t/RC}]$$

→ Transform domain

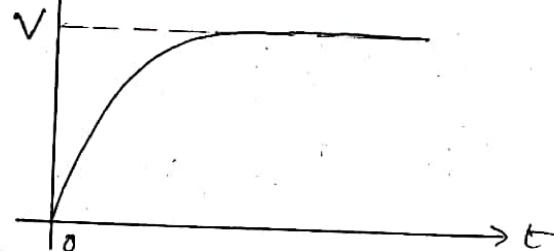
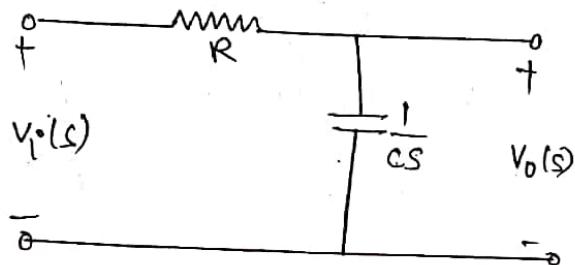



fig: Step response of RC low pass filter

$$V_o(s) = V_i(s) \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}}$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + RCS}$$

$$H(s=0) = 1.0$$

$$H(s=\infty) = 0.0$$

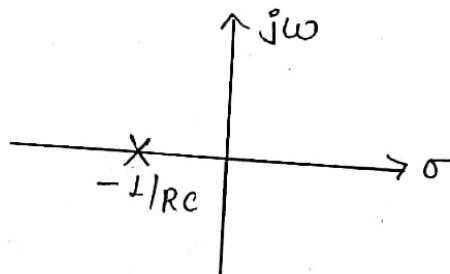

\* finite left hand pole in a s-plane represents first Order LPF.

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$H(j\omega) = \frac{1}{1 + j2\pi f RC}$$

$$H(j\omega) = \frac{1}{1 + j\omega/\omega_H}, \text{ where } \omega_H = \frac{1}{RC} \text{ rad/sec}$$

~~\*  $H(j\omega) = \frac{1}{1+j\omega/\omega_H}$  where  $\omega_H = \frac{1}{RC}$  rad/sec~~

~~\*  $H(j\omega) = \frac{1}{1+jF/f_H}$  where  $f_H = \frac{1}{2\pi RC}$  Hz.~~

$$|H(j\omega)| = \frac{1}{\sqrt{1+(F/f_H)^2}} = \text{Magnitude spectrum}$$

$$|H(j0)| = 1.0$$

$$|H(jf_H)| = \frac{1}{\sqrt{2}} = 0.707$$


$$|H(j\infty)| = 0.0$$

$$\angle H(j\omega) = -\tan^{-1}(F/f_H) = \text{Phase spectrum}$$

$$\angle H(j0) = 0^\circ$$

$$\angle H(jf_H) = -45^\circ$$

$$\angle H(j\infty) = -90^\circ$$

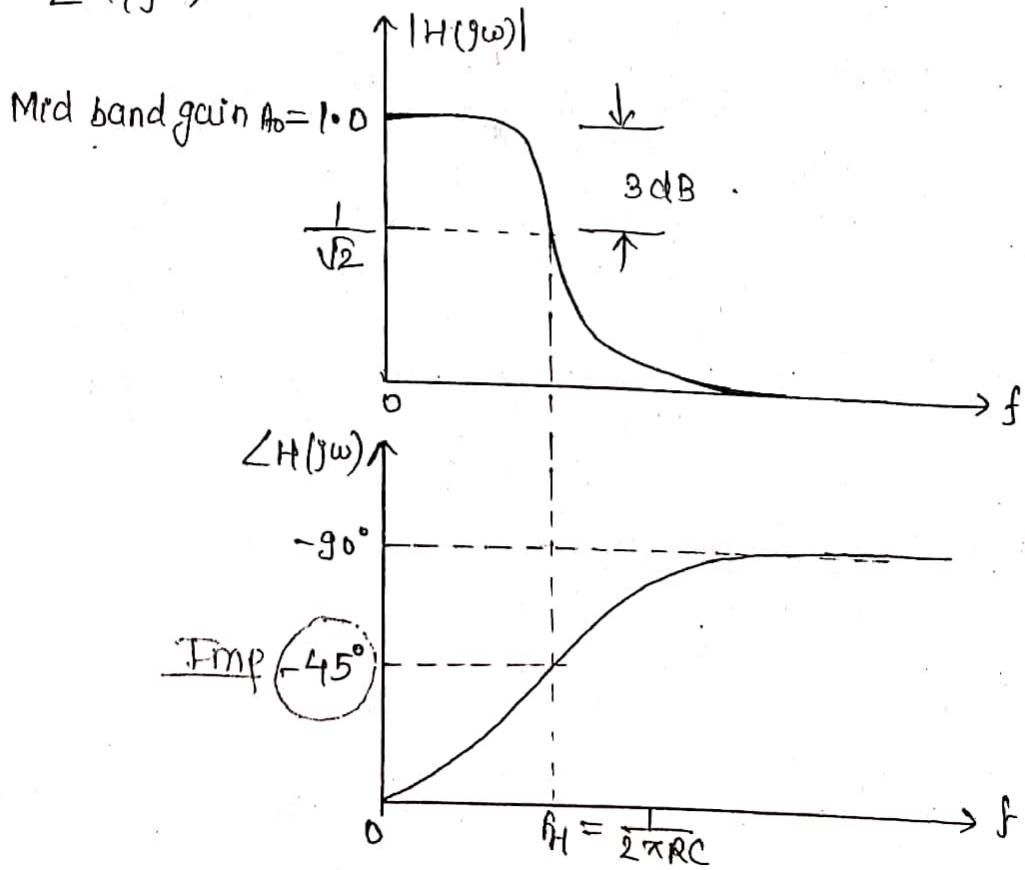

\* RC low pass filter is referred as Lagging Network or Lag compensator because it provides (-ve) angle for all positive values of frequency.

$$\rightarrow H(s) = \frac{1}{1+RCS}$$


Bode Plot :  $H(s) = \frac{1}{1+s/(1/RC)}$

$$K=1.0$$

$$\text{Corner freq } (\omega_c) = \frac{1}{RC} \text{ rad/sec}$$

$$\text{Pole} = \frac{1}{RC}$$

$$\text{Slope} = -20 \text{ dB/decade}$$

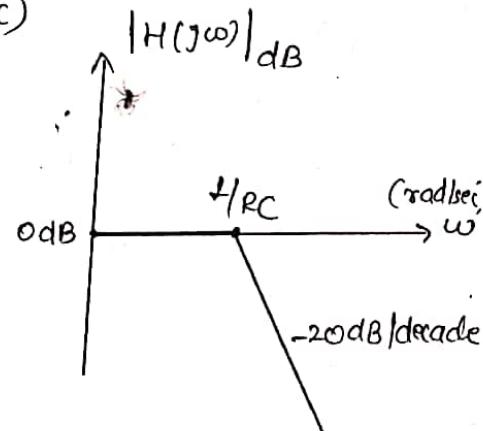

\* Analysis of Lower 3-dB Frequency :-

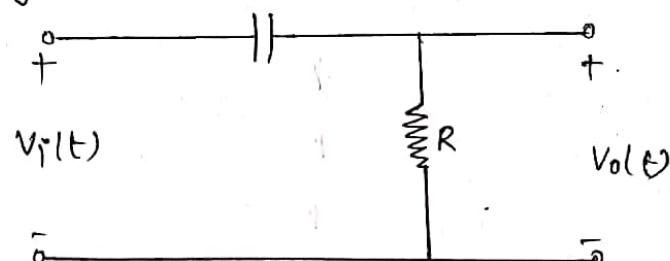


Fig:- RC Network

(i) Low Frequency

Ideal ( $f=0$ )

$$X_C = \infty$$


$$C = 0 \cdot C$$

(ii) High Frequency


Ideal ( $f=\infty$ )

$$X_C = \frac{1}{2\pi f C} = 0$$

$$C = S \cdot C$$


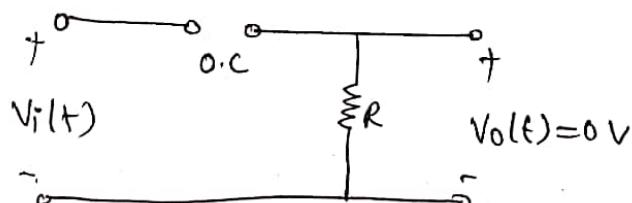


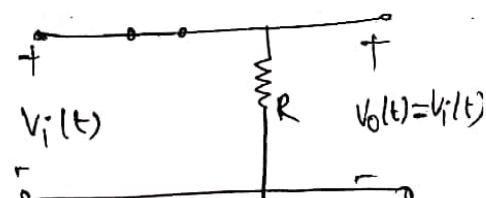∴ stops the low freq.  
i.e. s.t. no signal




∴ passes the high freq.  
i/p signal.

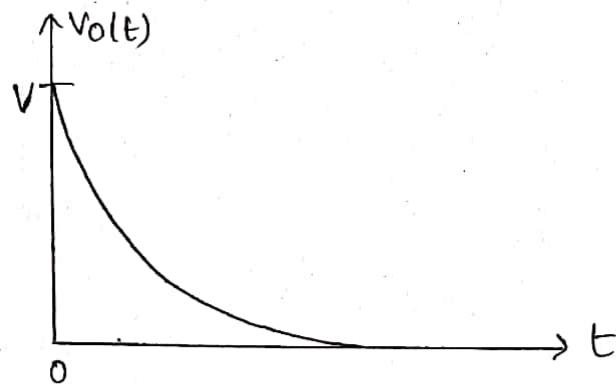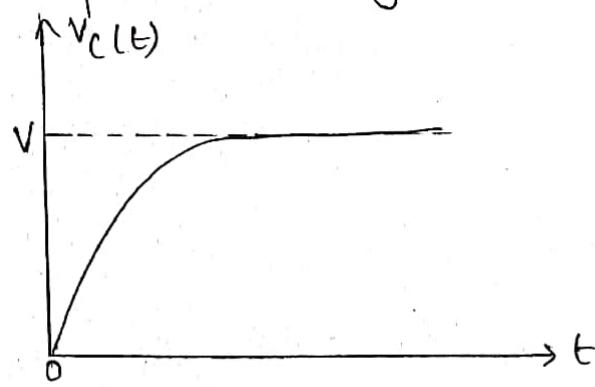∴ This Network represents High Pass Filter:-




Transform domain—

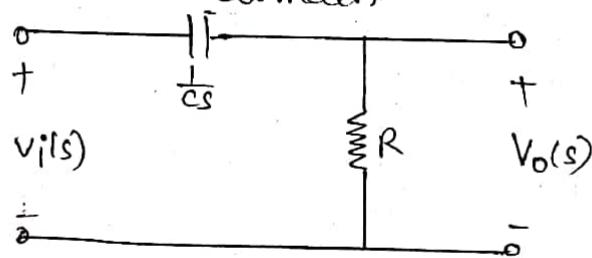

$$V_o(s) = V_i(s) \frac{R}{R + \frac{1}{cs}}$$
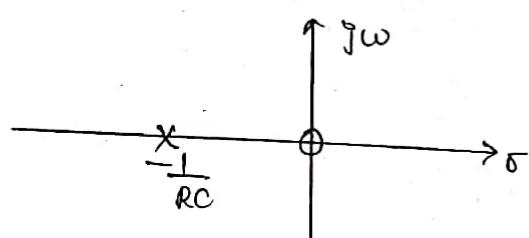
$$\boxed{\frac{V_o(s)}{V_i(s)} = H(s) = \frac{Rcs}{1 + Rcs}}$$



$$H(s=0) = 0 \cdot 0$$

$$H(s=\infty) = 1 \cdot 0$$

\* One 'zero' at origin and one left hand pole in S-plane represents a HPF.

$$H(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

$$H(j\omega) = \frac{1}{1 + \frac{1}{j\omega RC}}$$

$$H(j\omega) = \frac{1}{1 - j/\omega_{crossover}}$$

**WANT ECE BEST QUALITY-2019-20**

**LATEST HANDWRITING NOTES**

**BY**

**GATE ACADEMY CLICK HERE**

***Buy Now***

**Noted-:** Above ECE GATE/IES GATEACADEMY 2019-20

**CLASSROOM BEST QUALITY** Handwriting Notes Unique and Good Handwriting. Above Notes Enough for your Preparation.....

**Noted-:** Dear Aspirants If you do practice previous year paper 50% your work finished.so Guys daily at least 30minutes give previous year.

1. Previous year paper 4-5 times practice before final exam.
2. Subject wise study reference STD book
3. Test series practice more n more (Try to latest test series 2-3 fully solve then join online test series.)

**Noted-: Single Source Follow, Revise**

**Multiple Time Best key of Success**

$$H(j\omega) = \frac{1}{1 - j/2\pi FCR}$$

$$* H(j\omega) = \frac{1}{1 - j\omega_L/\omega} \quad \text{where } \omega_L = \frac{1}{RC} \text{ rad/sec}$$

$$* H(j\omega) = \frac{1}{1 - jF_L/f} \quad \text{where } F_L = \frac{1}{2\pi RC} \text{ Hz.}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (F_L/F)^2}}$$

$$\angle H(j\omega) = \tan^{-1}\left(\frac{F_L}{F}\right)$$

$$|H(j0)| = 0.0$$



$$\angle H(j0) = 90^\circ$$

$$|H(jF_L)| = \frac{1}{\sqrt{2}}$$

$$\angle H(jF_L) = 45^\circ$$

$$|H(j\infty)| = 1.0$$

$$\angle H(j\infty) = 0^\circ$$

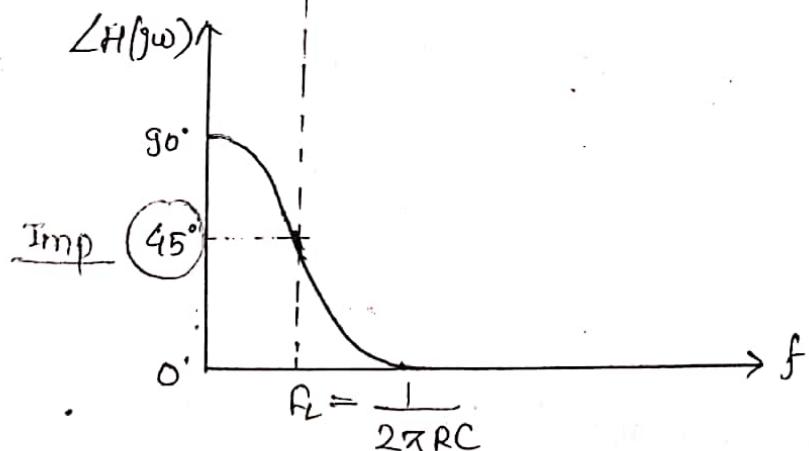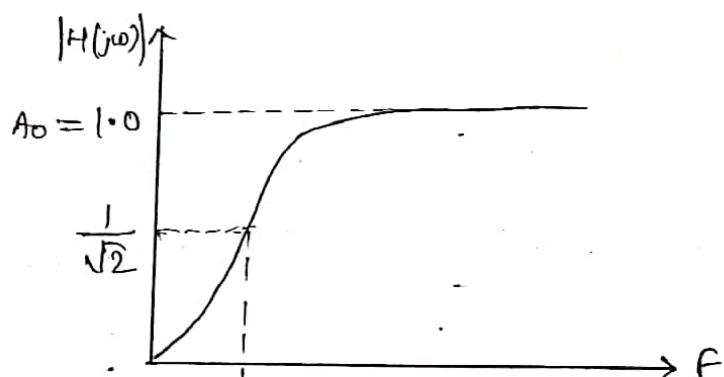

### Bode Plot:


$$H(s) = \frac{RCS}{1+RCS}$$

$$H(s) = \frac{RCS}{1+s/(1/RC)}$$

zero = origin, slope =  $20 \text{ dB/decade}$

Pole =  $-\frac{1}{RC}$ , slope =  $-20 \text{ dB/decade}$ .

$$K = RC$$

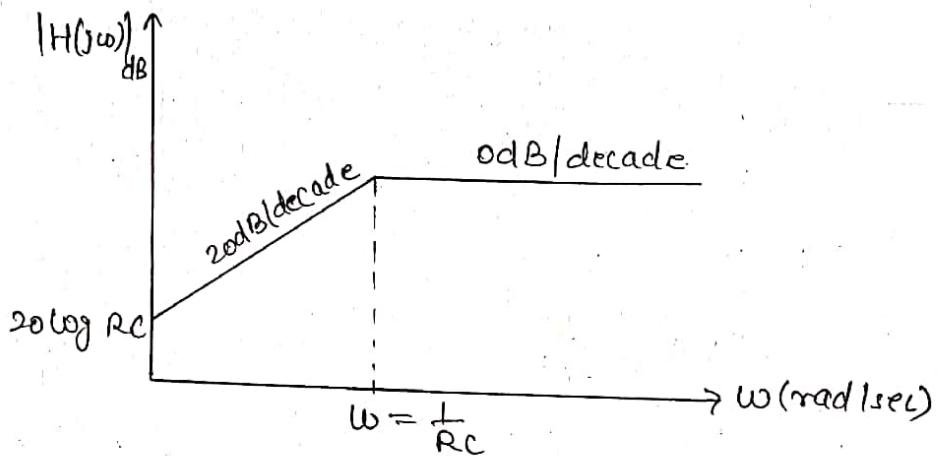

\* High pass filter is referred as Leading N( $\omega$ ) or Lead compensator.

\* Cascade Connection of Low and High pass filters:

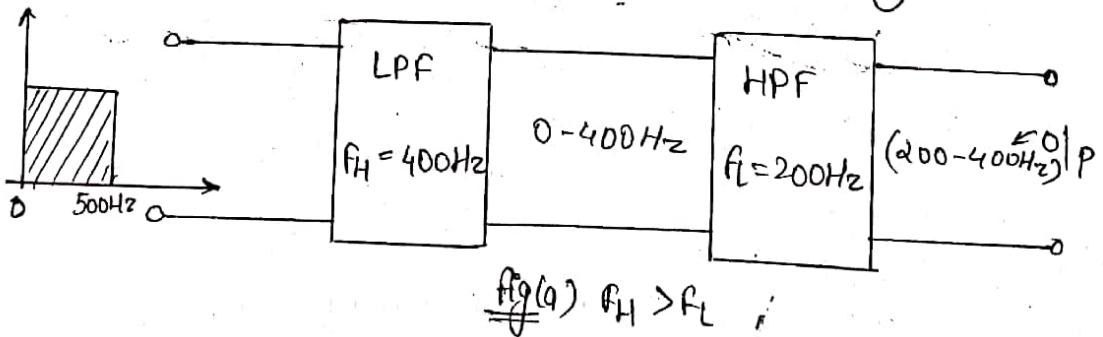


fig (a)  $f_H > f_L$

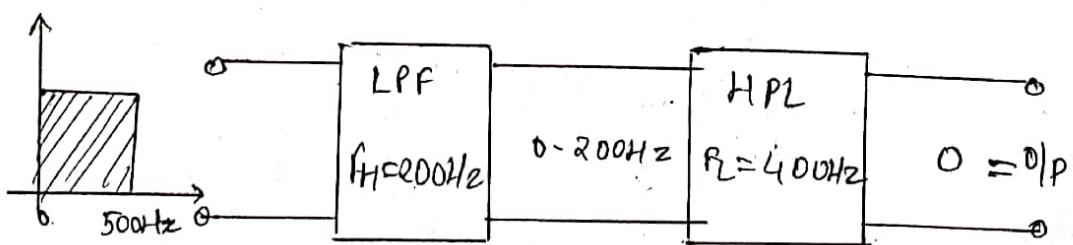


fig (b)  $f_L > f_H$

## CURRENT MIRROR CIRCUIT

The ckt in which the o/p current is forced to equal the i/p current is referred as Current Mirror ckt. (o/p current is mirror image of i/p current)


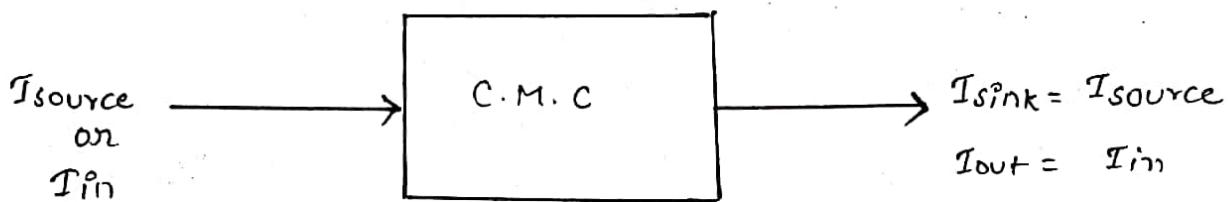


Fig Basic Block diagram.

Concept :-

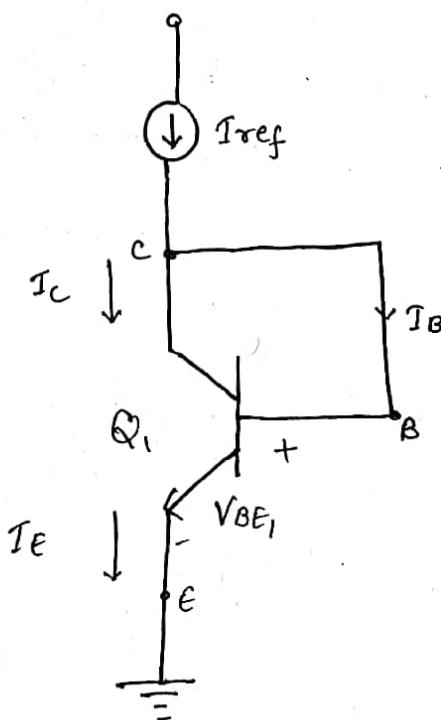

Fig, Diode connected Transistor  
( $V_{CB} = 0V$ )

$$V_{CB} = 0V$$

Assume:  $\beta = \text{very large}$

$$I_B = 0A$$


$$\text{i.e. } I_C = I_E = I_{ref}$$

$$I_{ref} = I_0 e^{\frac{V_{BE1}}{V_T}}$$

$$\frac{I_{ref}}{I_0} = e^{\frac{V_{BE1}}{V_T}}$$

$$\ln\left(\frac{I_{ref}}{I_0}\right) = \frac{V_{BE1}}{V_T}$$
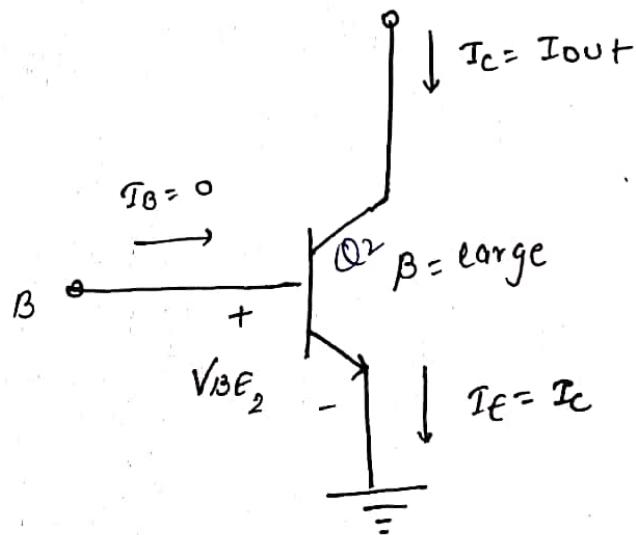
$$V_{BE1} = V_T \ln\left(\frac{I_{ref}}{I_0}\right) \quad \text{--- (1)}$$



$$I_{out} = I_0 e^{\frac{V_{BE2}}{V_T}}$$

$$\frac{V_{BE2}}{V_T}$$

$$\frac{I_{out}}{I_0} = e^{\frac{V_{BE2}}{V_T}}$$

**WANT ECE BEST QUALITY-2019-20**

**LATEST HANDWRITING NOTES**

**BY**

**GATE ACADEMY CLICK HERE**

***Buy Now***

**Noted-:** Above ECE GATE/IES GATEACADEMY 2019-20

**CLASSROOM BEST QUALITY** Handwriting Notes Unique and Good Handwriting. Above Notes Enough for your Preparation.....

**Noted-:** Dear Aspirants If you do practice previous year paper 50% your work finished.so Guys daily at least 30minutes give previous year.

1. Previous year paper 4-5 times practice before final exam.
2. Subject wise study reference STD book
3. Test series practice more n more (Try to latest test series 2-3 fully solve then join online test series.)

**Noted-: Single Source Follow, Revise**

**Multiple Time Best key of Success**

$$\ln \left( \frac{I_{out}}{I_0} \right) = \frac{V_{BE2}}{V_T}$$

$$V_{BE2} = V_T \ln \left( \frac{I_{out}}{I_0} \right) \quad \text{--- (2)}$$

if  $\underbrace{V_{BE1}}_{\sim} = \underbrace{V_{BE2}}_{\sim}$

$$V_T \ln \left( \frac{I_{ref}}{I_0} \right) = V_T \ln \left( \frac{I_{out}}{I_0} \right)$$

$$\frac{I_{ref}}{I_0} = \frac{I_{out}}{I_0}$$

$$I_{out} = I_{ref}$$

$I_{out} = I_{ref}$

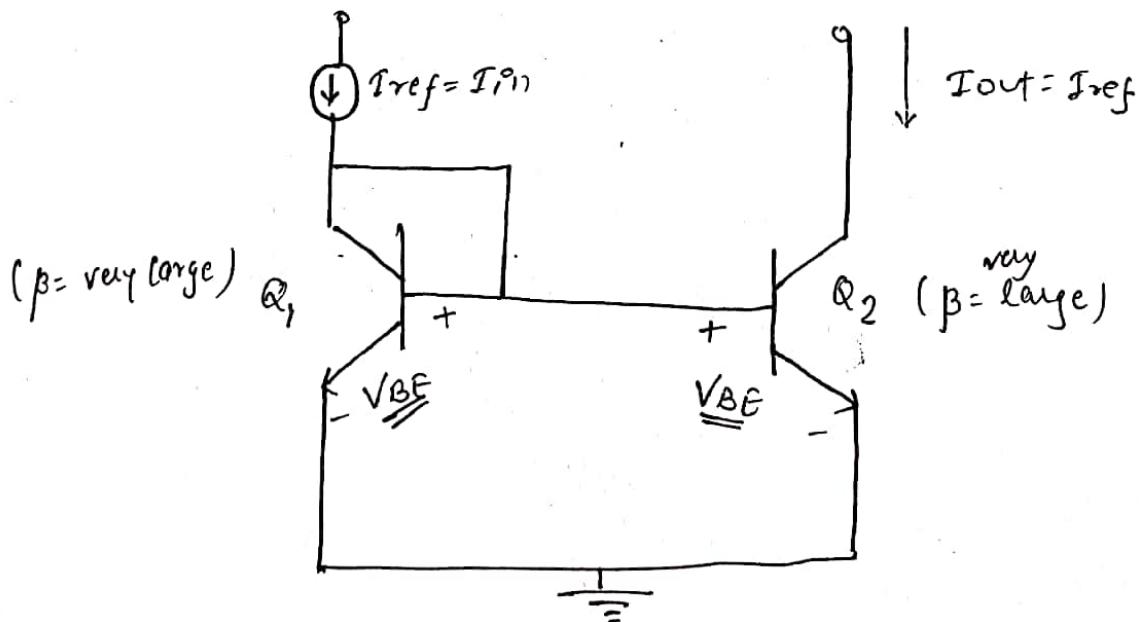


Fig Basic circuit diagram of C.M.C

Since the OIP current is mirror image of gip current therefore ckt is referred as current mirror ckt

### Requirement of Current Mirror ckt :-

- ① Both transistors should be in Active Region
- ② Both transistors should be identical or perfectly matched

$$2.1) V_{BE1} = V_{BE2} = V_{BE}$$

$$2.2) \beta_1 = \beta_2 = \beta \text{ (large)}$$

$$2.3) I_{B1} = I_{B2} = I_B$$

$$2.4) I_{C1} = I_{C2} = I_C$$

- ③ Emitter junction Area of both transistors should be identical

$$\text{Area } [J_{E1}] = \text{Area } [J_{E2}]$$

Notes

Reverse sat. current,  $I_o \propto$  Area of  $J_E$

$$I_E \propto I_o$$

$$I_E \propto \text{Area of } J_E$$

If there is no info. of Area of emitter junction then we assume identical Emitter & junction Area of both transistor

If  $\beta \neq \infty$

$I_B \neq 0A$

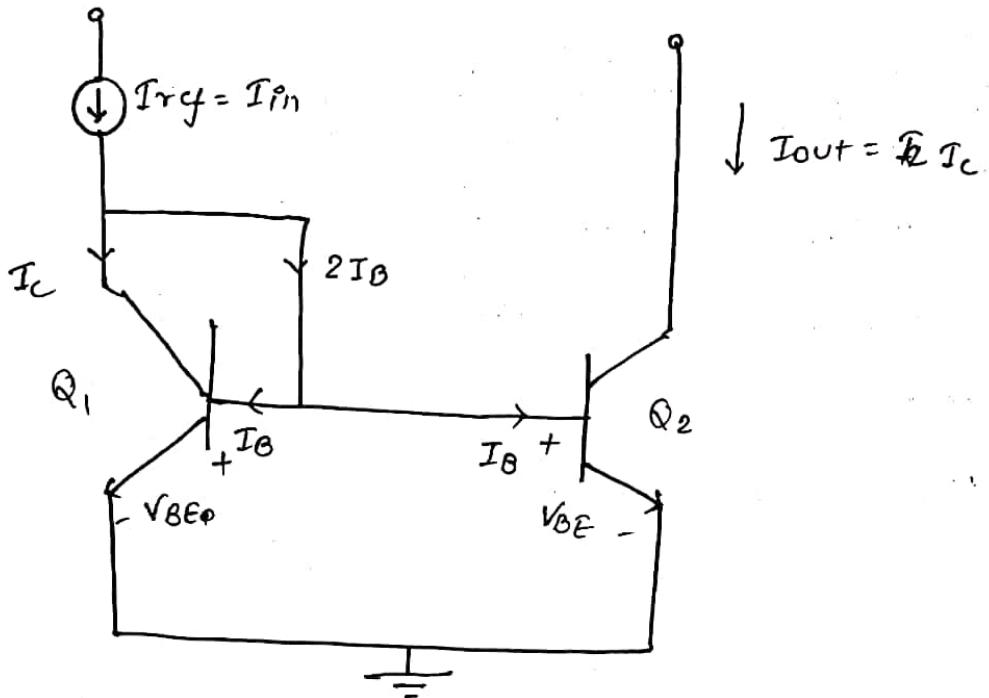


fig a)

From fig

$$I_{ref} = I_C + 2I_B$$

$$I_C [Q_1] = \beta I_B$$

$$I_{ref} = \beta I_B + 2I_B$$

$$I_{ref} = (\beta + 2) I_B$$

$$I_B [Q_2] = \frac{I_C}{\beta} = \frac{I_{out}}{\beta}$$

$$I_{ref} = (\beta + 2) \frac{I_{out}}{\beta}$$

$$I_{out} = \left( \frac{\beta}{\beta + 2} \right) I_{ref}$$

\*  
IMP

$$I_{out} = \left( \frac{\beta}{\beta + 2} \right) I_{ref}$$

i) if  $\beta = \infty$  then



$$I_{out} = I_{ref}$$

ii) if  $\beta \rightarrow \text{high}$

$$I_{out} \approx I_{ref}$$

Another form of Current Mirror Ckts

P.T.O

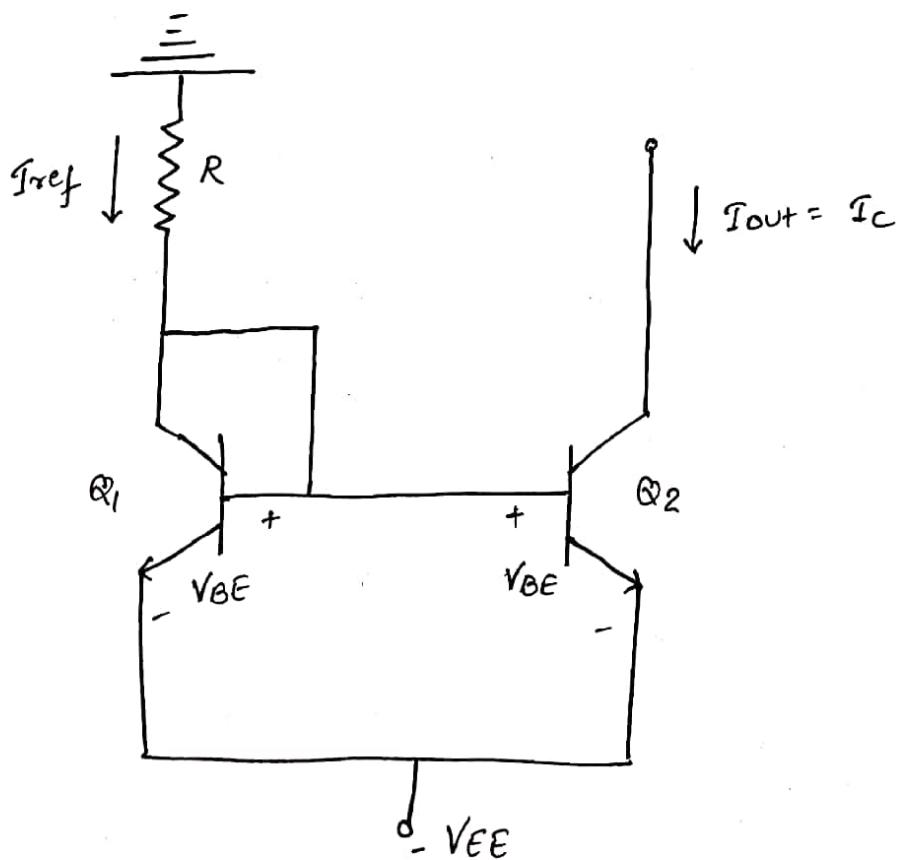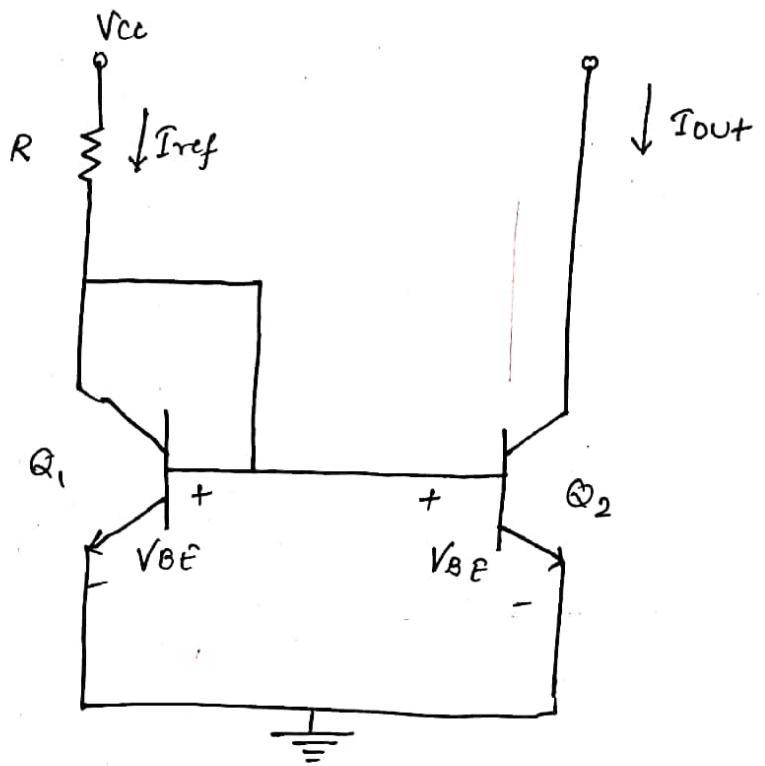

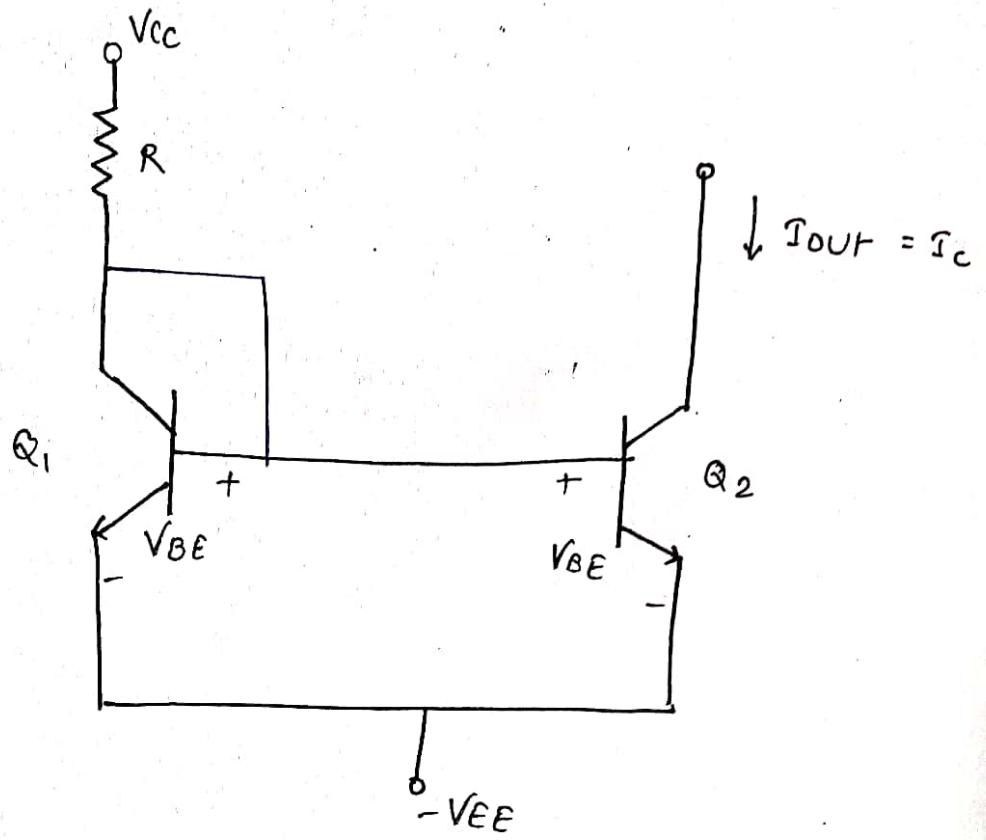


Fig d)

from fig b> :

$$V_{CC} = I_{ref}R + 0 + V_{BE} \quad \text{--- (1)}$$

$$I_{ref} = \frac{V_{CC} - V_{BE}}{R}$$

$$I_{out} = \left( \frac{\beta}{\beta+2} \right) I_{ref} \quad \underline{\text{Ans}}$$

from fig c>



$$O = I_{ref} R + O + V_{BE} - V_{EE}$$

$$I_{ref} = \frac{V_{EE} - V_{BE}}{R}$$

$$I_{out} = \left( \frac{\beta}{\beta+2} \right) I_{ref}$$

from fig d>

$$V_{cc} = I_{ref} R + O + V_{BE} - V_{EE}$$


$$I_{ref} = \frac{V_{cc} + V_{EE} - V_{BE}}{R}$$

$$I_{out} = \left( \frac{\beta}{\beta+2} \right) I_{ref}$$

$\beta$	$I_{out} = \left( \frac{\beta}{\beta+2} \right) I_{ref}$
5	0.714 $I_{ref}$
10	0.83 $I_{ref}$
50	0.96 $I_{ref}$

Conclusion:

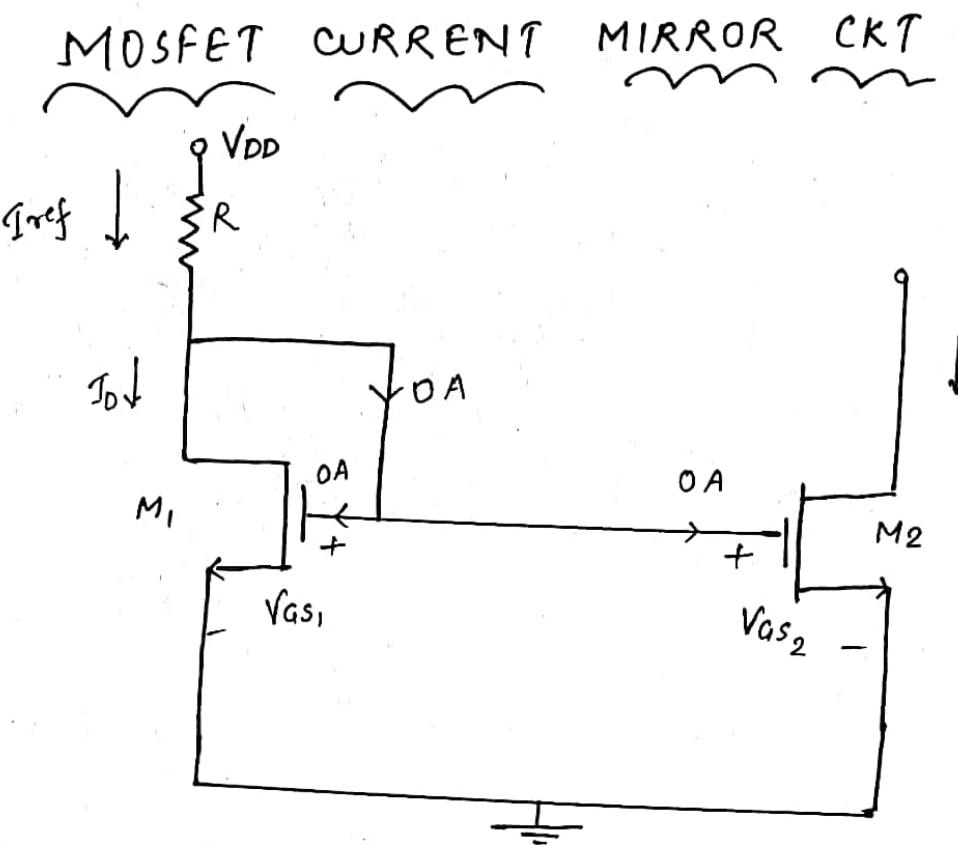for small value  
of  $\beta$   $I_{out}$  is  
not mirror image  
of  $I_{ref}$



When  $V_{DG} = 0$  then

$$V_{DS} > V_{GS} - V_{TN} = V_{ov}$$

i.e NMOS  $\rightarrow$  saturation Region.

$M_1$  = saturation Region

$$I_{D1} = I_{D2}$$

$$I_{D1} = I_{out}$$

$$k_{n1} [V_{GS1} - V_{TN1}]^2 = k_{n2} [V_{GS2} - V_{TN2}]^2$$

$I_{D1}$  and  $I_{D2}$  are equal only if

- i)  $k_{n1} = k_{n2}$
  - ii)  $V_{TN1} = V_{TN2}$
  - iii)  $V_{ov1} = V_{ov2}$
- } then only  $I_{out} = I_{ref}$

# Operational Amplifier (Op-Amp)

1. Op-amp is a high gain DC amplifier (Direct Coupled Amp) which can perform some Mathematical operation like addition, subtraction, Multiplication, division, Integration, differentiation, log, anti log etc.
2. Op-amp Can amplify both DC and AC Signal from 0 to  $10^6$  Hz.
- \* 3. Op-amp is referred as Voltage Controlled Voltage Source device

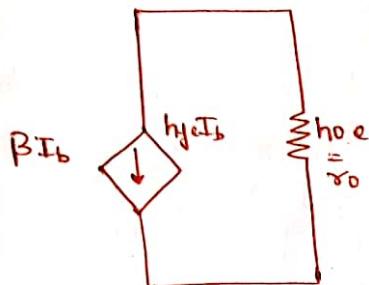


fig. BJT (CCCS)

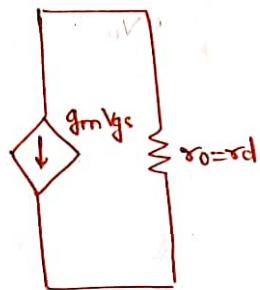


fig. JFET/Mosfet (VCCS)

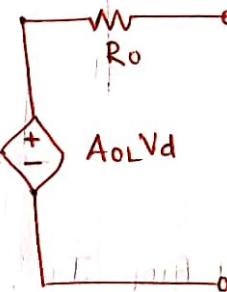


fig. Opamp [VCVS]

## 4. Symbolic Representation

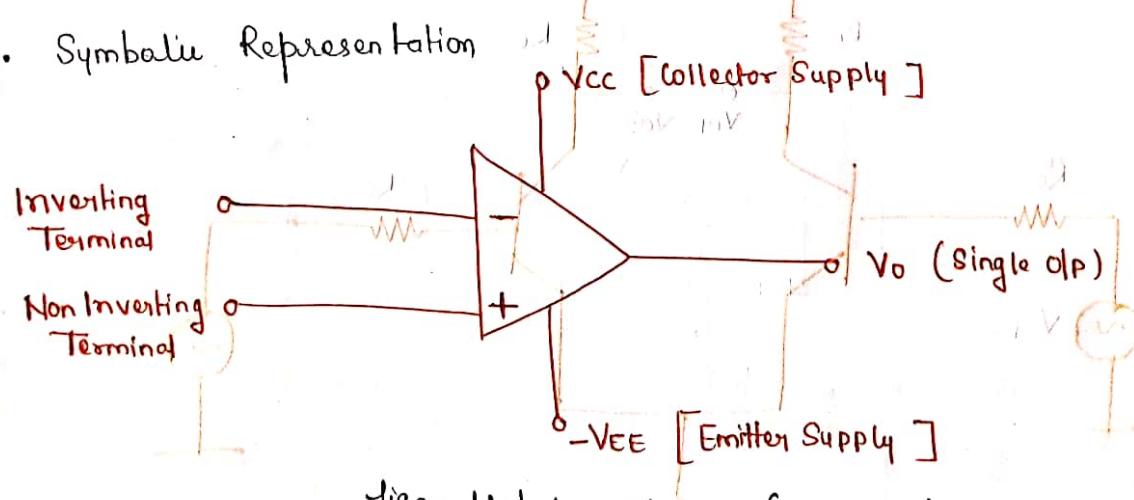


fig.a. Unbalanced o/p (Single o/p) op-amp.


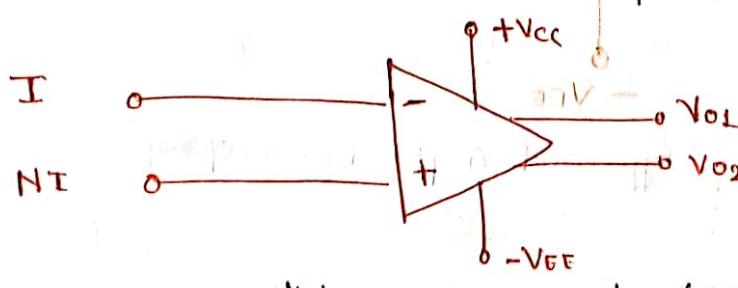



fig.b. Balanced o/p (Two o/p) opamp.

$$V_{cc} = -V_{EE}$$

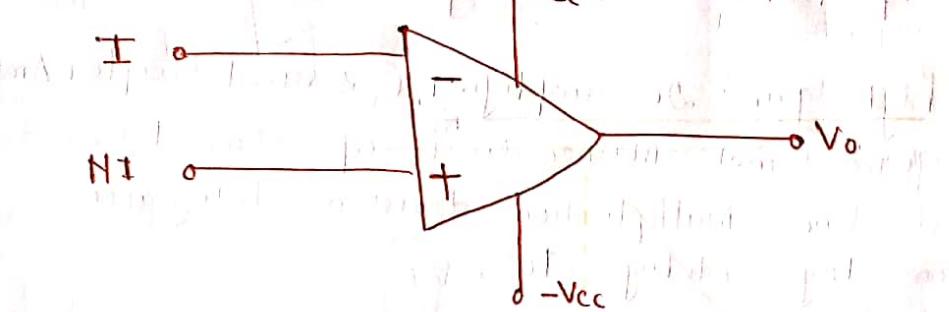

fig(c)

e.g.

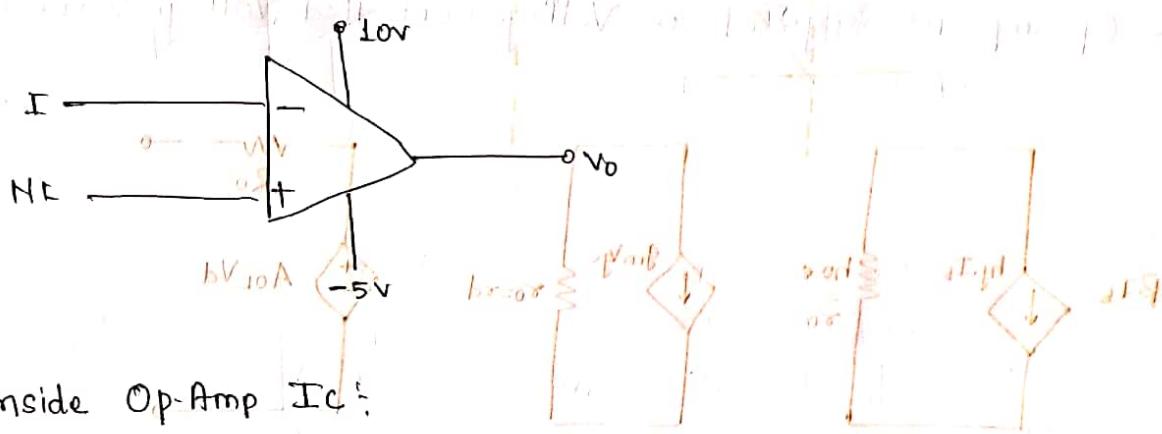

Inside Op-Amp IC:


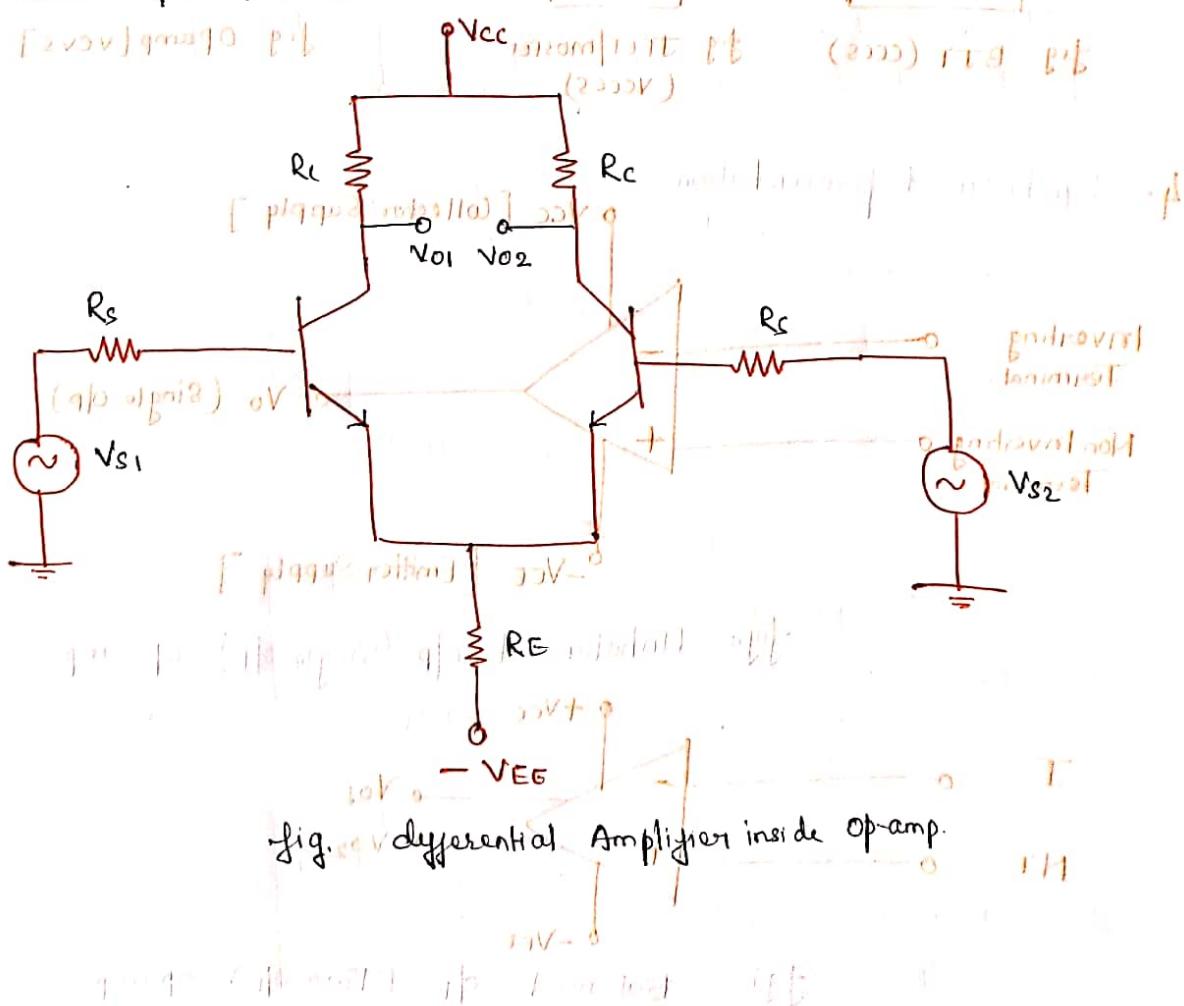


fig. (e) v differential Amplifier inside Op-amp.

## 5: Transfer characteristic

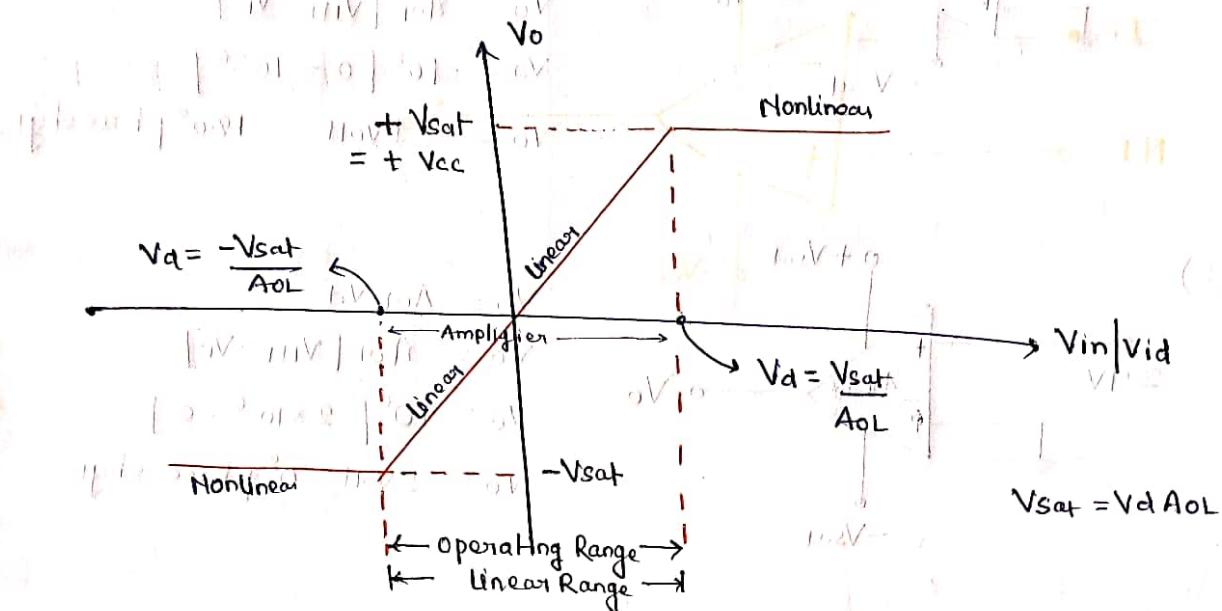


$$\text{Maximum positive Output Voltage} = +V_{sat}$$

$$\text{Maximum Negative Output Voltage} = -V_{sat}$$

$$V_{in} = \text{Input Voltage} = V_{NI} - V_E$$


$$V_d = \text{difference Voltage} = V_{NI} - V_E$$

$$V_{in} = V_d = V_{NI} - V_E$$

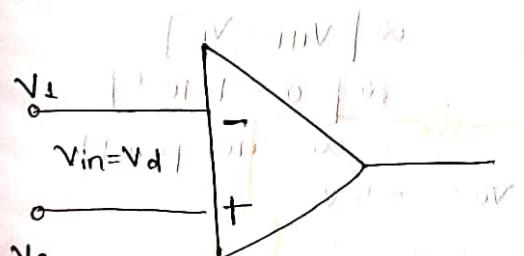

$$\text{fig. } V_d = V_{NI} - V_E$$

$$V_d = V_2 - V_1$$

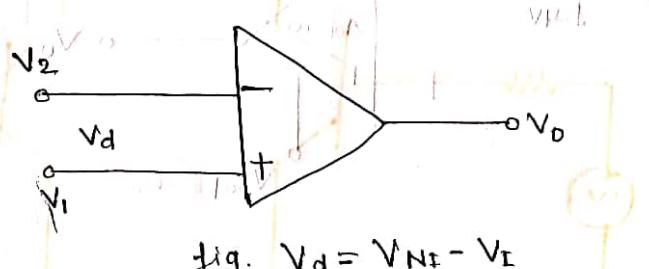

$$\text{fig. } V_d = V_{NI} - V_E$$


$$V_d = V_1 - V_2$$

if  $V_d > +V_{sat}$

$$\boxed{-\frac{V_{sat}}{A_O L} < V_d < \frac{V_{sat}}{A_O L}}$$

$\rightarrow$  for operation in Linear Region

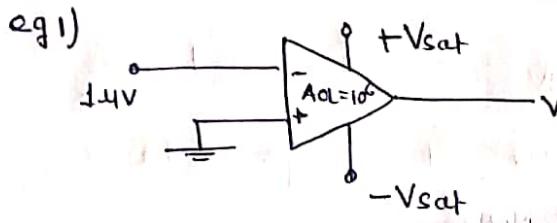$\rightarrow$  above that Range Op-amp Saturates




$$V_o = A_{OL} V_d$$

$$V_o = A_{OL} [V_{NI} - V_t]$$

$$V_o = 10^6 [0 - 10^{-6}]$$
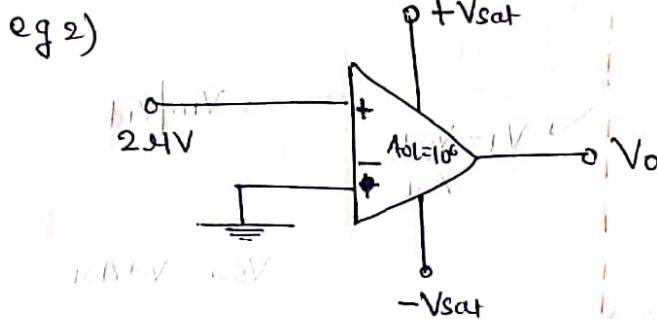
$$V_o = 10 \text{ volt } 180^\circ \text{ phase shift}$$




$$V_o = A_{OL} V_d$$

$$V_o = A_{OL} [V_{NI} - V_t]$$

$$V_o = 10^6 [2 \times 10^{-6} - 0]$$
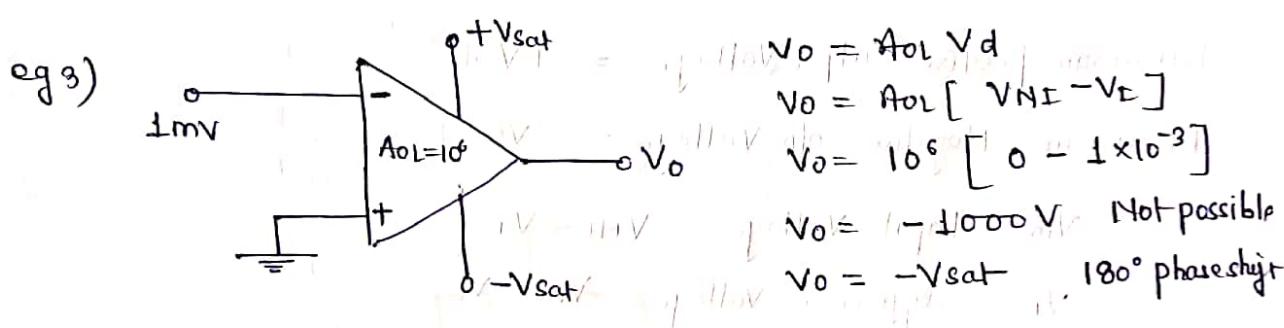
$$V_o = 2 \text{ volt } 0^\circ \text{ phase shift}$$




$$V_o = A_{OL} V_d$$

$$V_o = A_{OL} [V_{NI} - V_t]$$

$$V_o = 10^6 [0 - 1 \times 10^{-3}]$$

$$V_o = -1000 \text{ V Not possible}$$
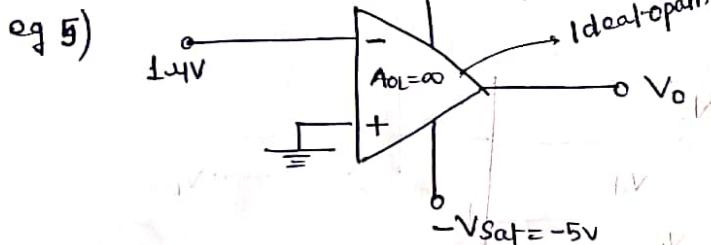
$$V_o = -Vsat \text{ } 180^\circ \text{ phase shift}$$




$$V_o = A_{OL} V_d$$

$$= \infty [V_{NI} - V_t]$$

$$= \infty [0 - 1 \times 10^{-6}]$$

$$= -\infty \text{ not possible}$$

$$V_o = -5 \text{ V}$$

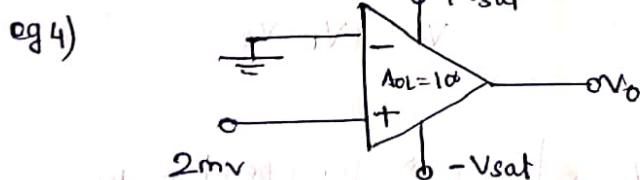


$$V_o = A_{OL} [V_{NI} - V_t]$$

$$= 10^6 [2 \times 10^{-3} - 0]$$

$$= 2000 \text{ Not possible}$$

$$V_o = +Vsat$$

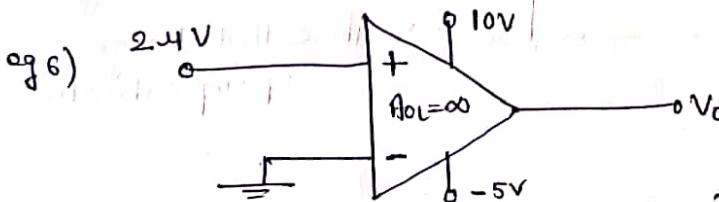

$$V_o = A_{OL} V_d$$

$$= A_{OL} [V_{NI} - V_t]$$



$$= \infty [2 \times 10^{-6} - 0]$$

$$= \infty \text{ Not possible}$$

$$V_o = 10 \text{ V}$$

Key point:- If there is no information of op-amp then by default we assume Ideal Opamp that means  $A_{OL} = \infty$ .

e.g 7)

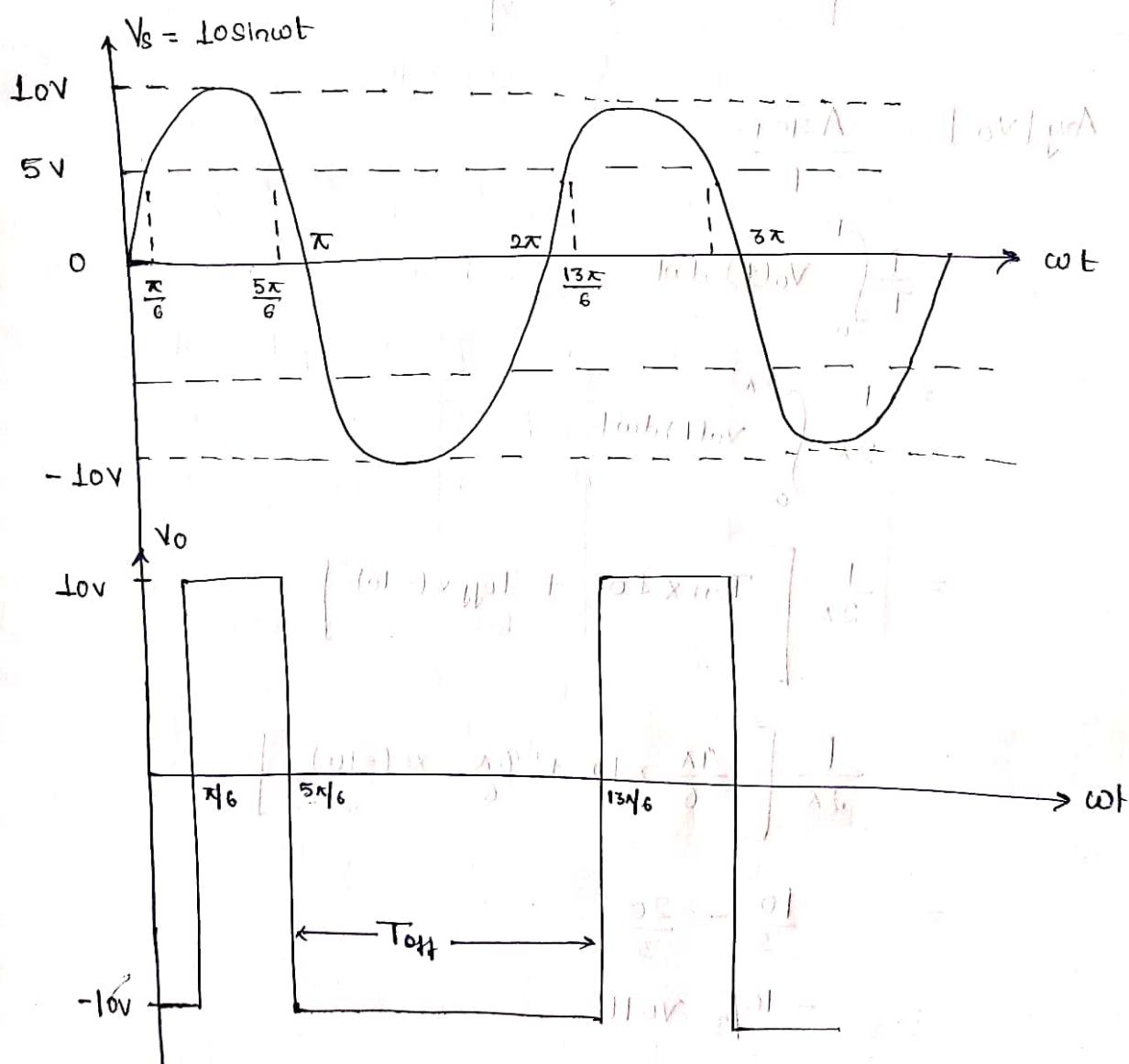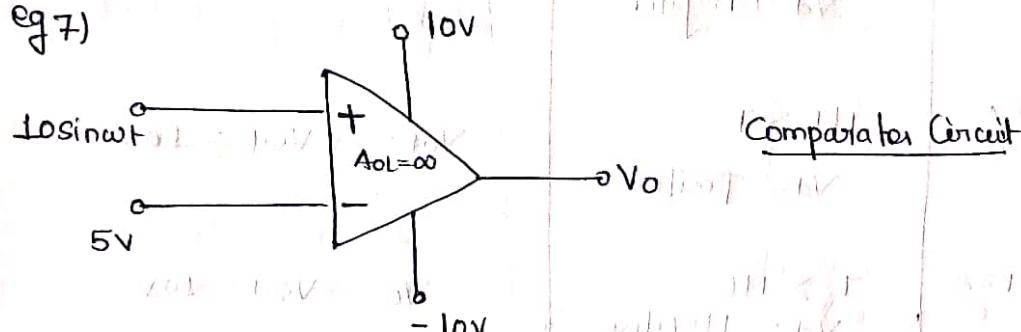

Time period of  $1/f_p = 2\pi$

Time period of  $0/f_p = 2\pi$

**WANT ECE BEST QUALITY-2019-20**

**LATEST HANDWRITING NOTES**

**BY**

**GATE ACADEMY CLICK HERE**

***Buy Now***

**Noted-:** Above ECE GATE/IES GATEACADEMY 2019-20

**CLASSROOM BEST QUALITY** Handwriting Notes Unique and Good Handwriting. Above Notes Enough for your Preparation.....

**Noted-:** Dear Aspirants If you do practice previous year paper 50% your work finished.so Guys daily at least 30minutes give previous year.

1. Previous year paper 4-5 times practice before final exam.
2. Subject wise study reference STD book
3. Test series practice more n more (Try to latest test series 2-3 fully solve then join online test series.)

**Noted-: Single Source Follow, Revise**

**Multiple Time Best key of Success**

$\omega t$	$V_d = V_{H1} - V_I$	$V_o = A_{OL} V_d$
$0 < \omega t < \frac{\pi}{6}$	$I > Nt$ $V_d = \text{Negative}$	$V_o = -V_{sat} = -10V$
$\frac{\pi}{6} < \omega t < \frac{5\pi}{6}$	$Nt > I$ $V_d = \text{Positive}$	$V_o = +V_{sat} = 10V$
$\frac{5\pi}{6} < \omega t < \frac{13\pi}{6}$	$I > Nt$ $V_d = \text{Negative}$	$V_o = -V_{sat} = -10V$

$$\text{Avg}[V_o] = \frac{A_{OL} q_{eq}}{T}$$

$$= \frac{1}{T} \int_0^T V_o(t) d\omega t$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_o(t) d\omega t$$

$$= \frac{1}{2\pi} \left[ T_{ON} \times 10 + T_{OFF} \times (-10) \right]$$

$$= \frac{1}{2\pi} \left[ \frac{4\pi}{6} \times 10 + \frac{8\pi}{6} \times (-10) \right]$$

$$= \frac{10}{3} - \frac{20}{3}$$

$$= -10/3 \text{ volt}$$

Duty cycle =

$$\frac{T_{ON}}{T} \times 100\%$$

$$= \frac{T_{ON}}{T_{ON} + T_{OFF}} \times 100 = \frac{\frac{4\pi}{6}}{\frac{4\pi}{6} + \frac{8\pi}{6}} \times 100 = 33.33\%$$

Note:

①  $T_{on} < T_{off}$

$\% \Delta < 50\%$

Avg [vo] = Negative

Rectangular waveform

②  $T_{on} > T_{off}$

$\% \Delta > 50\%$

Avg [vo] = Positive

Triangle waveform


③  $T_{on} = T_{off}$

$\% \Delta = 50\%$


Avg [vo] = zero

Square waveform

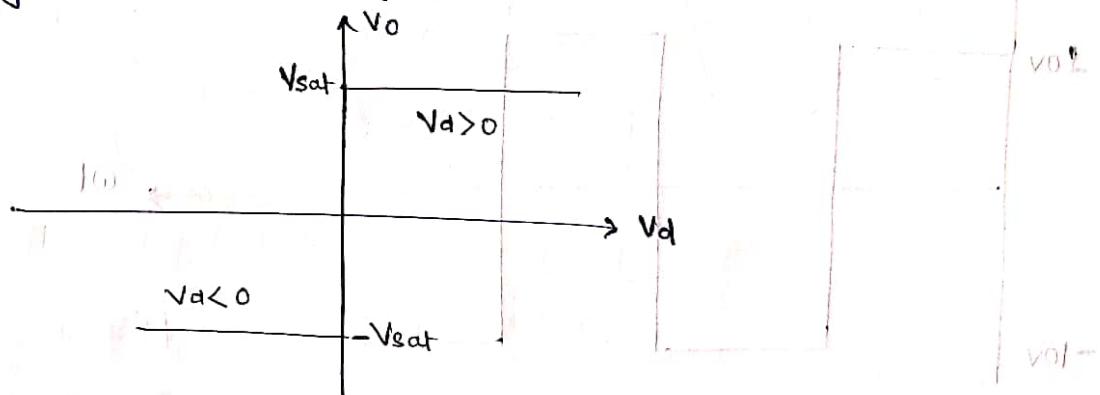Transfer characteristics of Ideal opamp. (Comparator Circuit)



e.g. ⑥

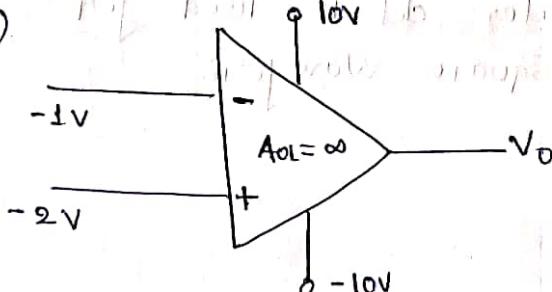

Sol  $V_o = -10V$

$T > NI$

$V_o = -V_{sat} = -10V$

$V_o = A_{OL} V_d$

$= A_{OL} [-2 + 1]$

$= -\infty$

$V_o = -10V$

eq(g)



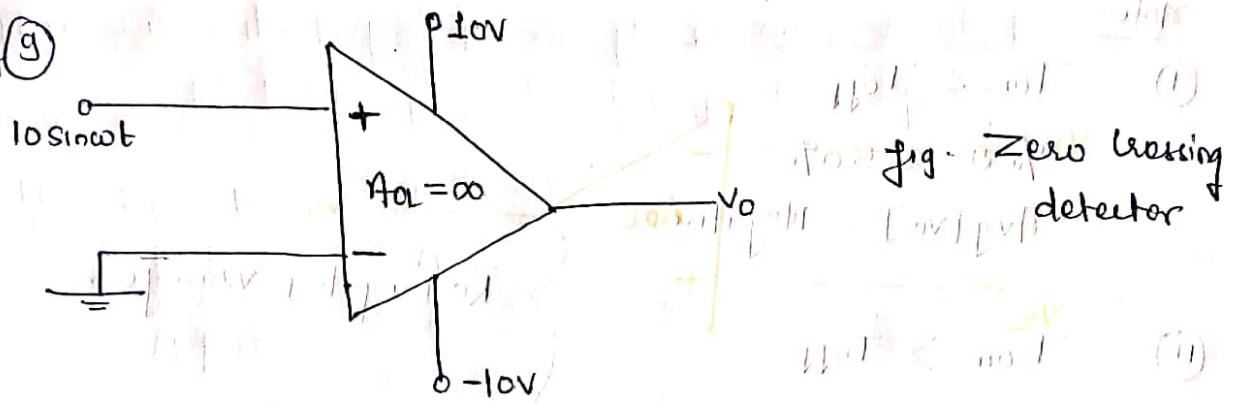


fig - Zero crossing detector

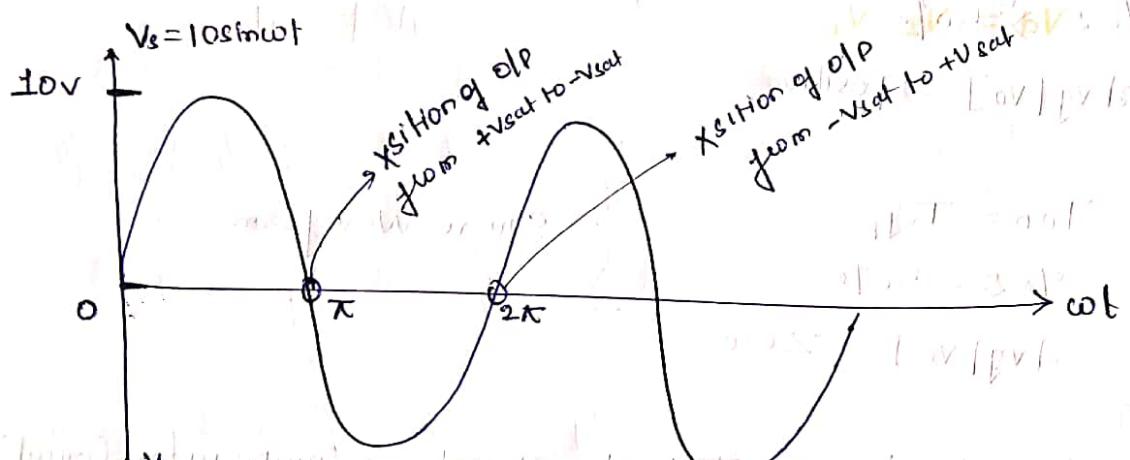

(m)

$V_o = 10\sin\omega t$

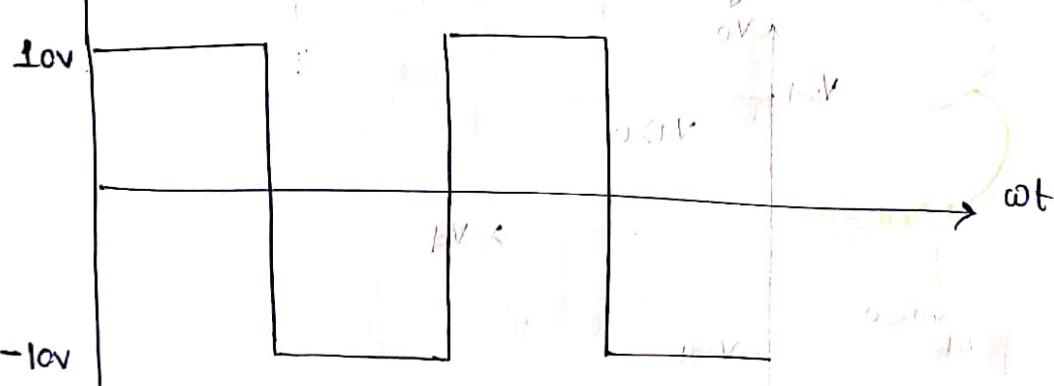


Keypoint: Zero crossing detector circuit is used for generation of Square Waveform.

(GP)

$V_o = 10\sin\omega t$

## \* Virtual Ground Concept

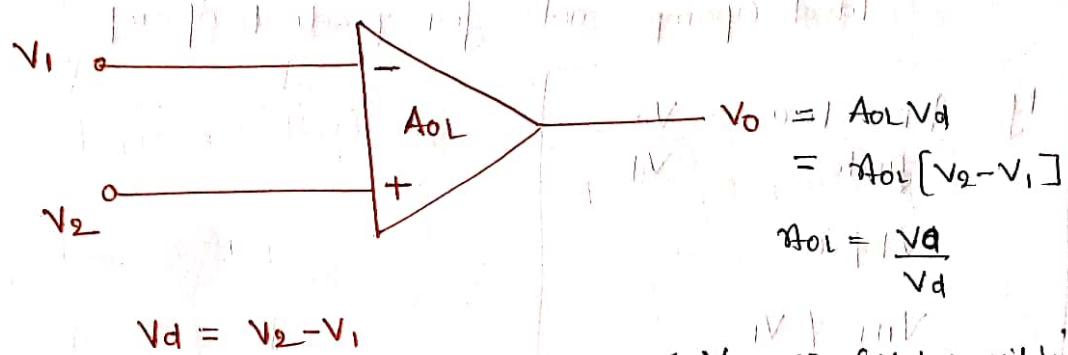

Ideal opamp :-  $A_{OL} = \infty$

$$V_o = \infty \text{ (Not possible)}$$


$$V_o = \pm V_{sat}$$

$$V_o = 0 \text{ (possible)}$$


$$V_d = 0$$

$V_2 - V_1 = 0$  (both  $V_1$  and  $V_2$  are at  $0V$ )

$$V_2 = V_1$$


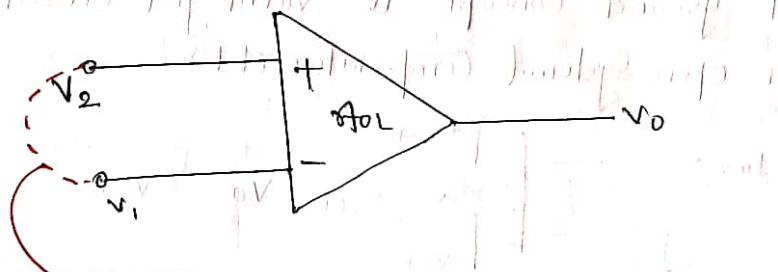


$$\text{eq } ① \quad V_E = V_{HE} = 0V$$

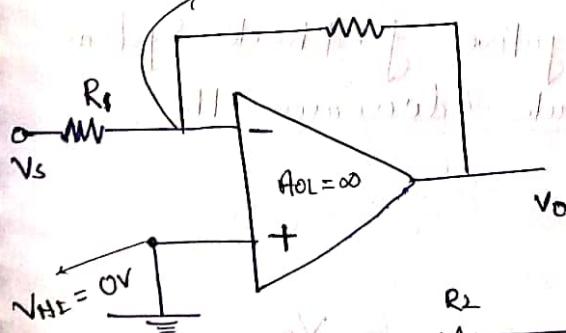

$$V_I = V_{HE} = V_s$$
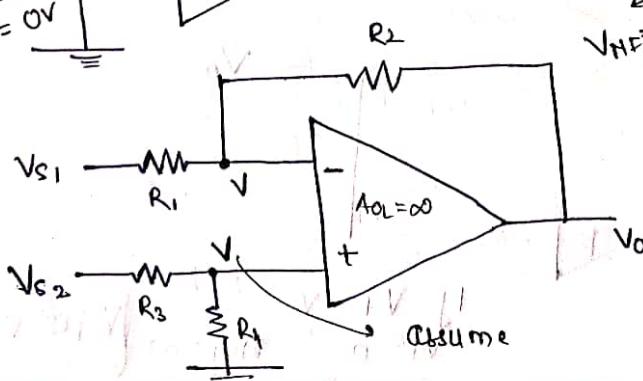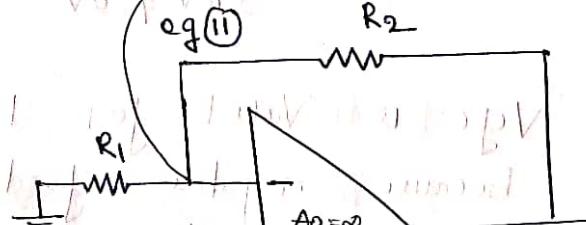
$$\text{eq } ② \quad V_E = V_{HE} = V_s$$






## \* Amplifier

Case 1

Source

Dc Supply

Load

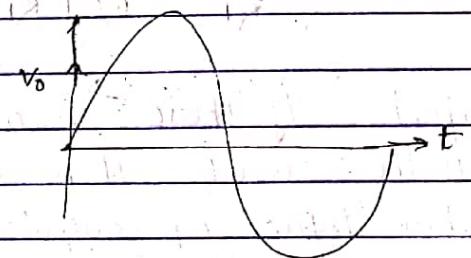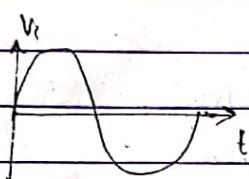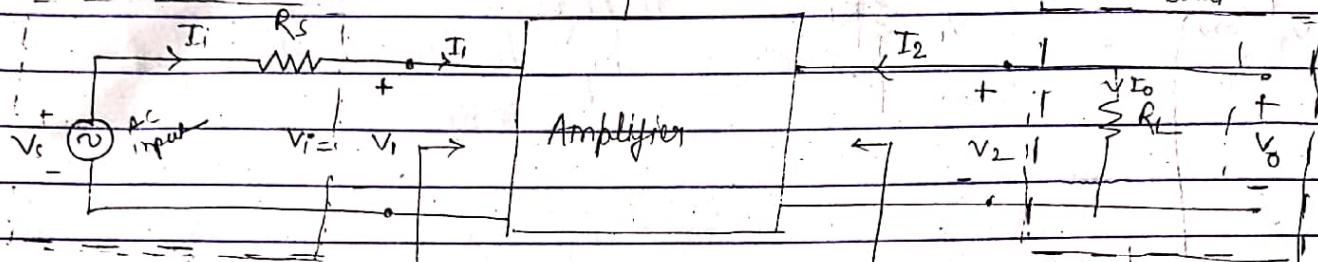


- Amplifier is a device which increases power level of input signal  
i.e. Amplification or Boosting of input signal
- For amplifying we use mostly BJT, TFT & Mosfet
- For amplifying device should be in proper region
- For amplifying BJT should be in active region
- For amplifying TFT & Mosfet should be in saturation region
- Dc Supply maintain the region of device for amplifying
- Internal Input Impedance is given by:

$$R_i = \frac{V_i}{I_i}$$

from fig.  $R_i = \frac{V_i}{I_i}$

- Total Input resistance of amplifier is given by  
(Input Resistance seen from Th. Source)

$$R_i' = \frac{V_s}{I_i} = R_s + R_i$$

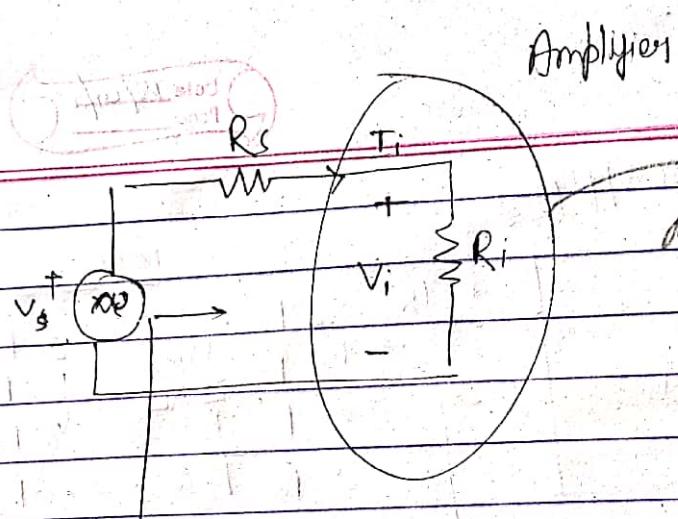


The whole  
Amplifier is Replaced  
by its Internal Input  
Impedance

$$R_i' = R_s + R_i = \frac{V_s}{I_i}$$

keypoint: If there is no information of position of arrow in the circuit then we will consider total resistance either input or output

$$\frac{V_{ce}}{R_c}$$

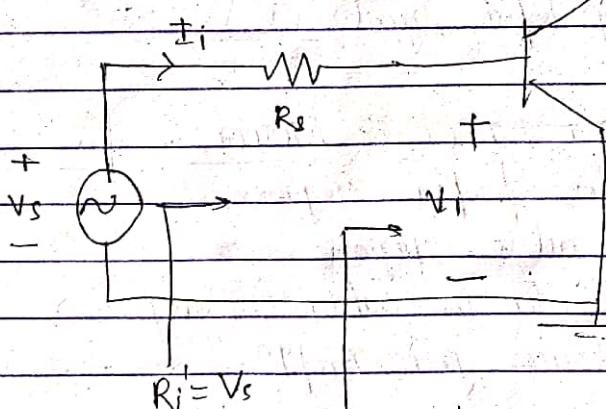


$$R_i' = \frac{V_s}{I_i}$$

Total  
Input  
Impedance

$$R_i = \frac{V_i}{I_i}$$

Internal Input Resistance

$$\frac{V_o}{I_o}$$

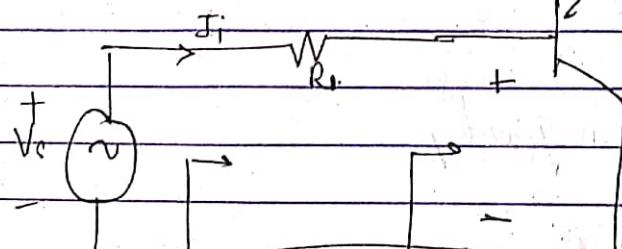

$$\text{Total Input Imp. } R_i = \frac{V_s}{I_i}$$


$$R_i' \text{ Internal Input Imp.}$$

Internal output resistance is given by

$$R_o = \frac{V_2}{I_2} \quad \Rightarrow R_o \text{ is shown Resistance}$$

$V_s = 0$

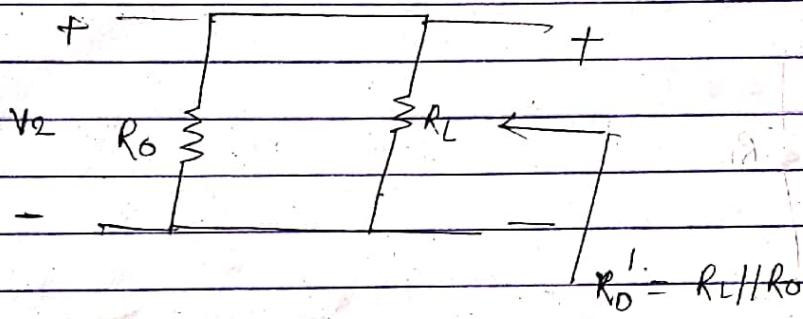Total output resistance of Amplifier is given by



Internal Voltage gain of Amplifier is given by

$$A_v = \frac{V_2}{V_1} \quad \begin{array}{l} \text{Internal output Volts} \\ \text{Internal Input Volts} \end{array}$$

from figure.  $V_2 = V_o$ ,  $V_1 = V_i$

In o/p. got case  $V_2 = V_o$

$$A_v = \frac{V_o}{V_i} \quad \begin{array}{l} \text{(only dual of Miller Amp)} \\ \text{has } V_2 = V_o \end{array}$$

but it is conventional

Overall Voltage gain or Total Volts gain of Amp is given by

$$A_{Vs} = \frac{V_o}{V_s} = \frac{\text{output Volts}}{\text{source Volts}}$$

**WANT ECE BEST QUALITY-2019-20**

**LATEST HANDWRITING NOTES**

**BY**

**GATE ACADEMY CLICK HERE**

***Buy Now***

**Noted-:** Above ECE GATE/IES GATEACADEMY 2019-20

**CLASSROOM BEST QUALITY** Handwriting Notes Unique and Good Handwriting. Above Notes Enough for your Preparation.....

**Noted-:** Dear Aspirants If you do practice previous year paper 50% your work finished.so Guys daily at least 30minutes give previous year.

1. Previous year paper 4-5 times practice before final exam.
2. Subject wise study reference STD book
3. Test series practice more n more (Try to latest test series 2-3 fully solve then join online test series.)

**Noted-: Single Source Follow, Revise**


**Multiple Time Best key of Success**

This Voltage gain is also referred as Voltage gain with  
Source resistance.

Date \_\_\_\_\_  
Page \_\_\_\_\_

$$A_{Vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s}$$

$$A_{Vs} = A_v \times V_i$$

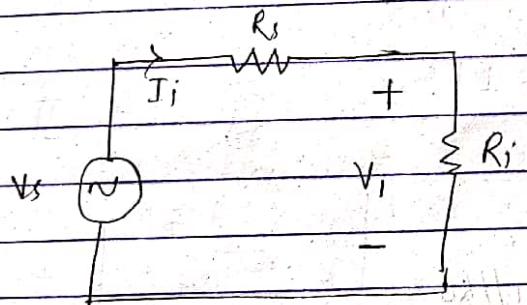

$$V_i = \frac{V_s R_i}{R_i + R_s}$$


$$\frac{V_i}{V_s} = \frac{R_i}{R_i + R_s}$$

$$A_{Vs} = A_v \frac{R_i}{R_i + R_s}$$

$$A_{Vs} < A_v$$

$$\frac{R_i}{R_i + R_s} < 1$$

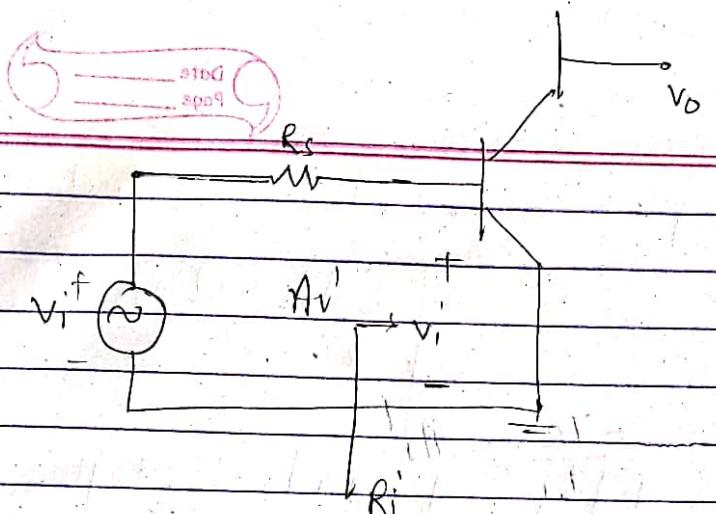Overall Voltage gain will always less than Internal Voltage gain.



$$AV = \frac{V_o}{V_i} = ? \quad \text{total internal volt gain}$$

$$AV = AV \frac{R_L}{R_i + R_L}$$

Practical Volt. Source

has Internal Resistor  
in Series which is  
Very small

- If  $R_s = 0$

then  $V_s = \text{ideal Volt. Source}$

$$AV_s = AV \frac{R_L}{R_s + R_L} \quad R_s = 0 \quad | \quad AV_s < AV$$

$| \quad AV_s = AV$

Internal Current gain of Amplifier is given by

$$A_i' = -\frac{I_2}{I_1}$$

where  $I_2 = \text{output twoport current}$

$I_1 = \text{input port current}$

Overall Current gain is given by

$$A_i = I_o = \frac{\text{Output Load Current}}{\text{Input Source Current}}$$

from figure


$$I_0 = -I_2$$

$$I_L = I_i$$

Overall Current gain =  $\frac{I_0}{I_i} = \frac{-I_2}{I_i} = A_I^1$


Case II :-

$$I_L \neq I_i$$

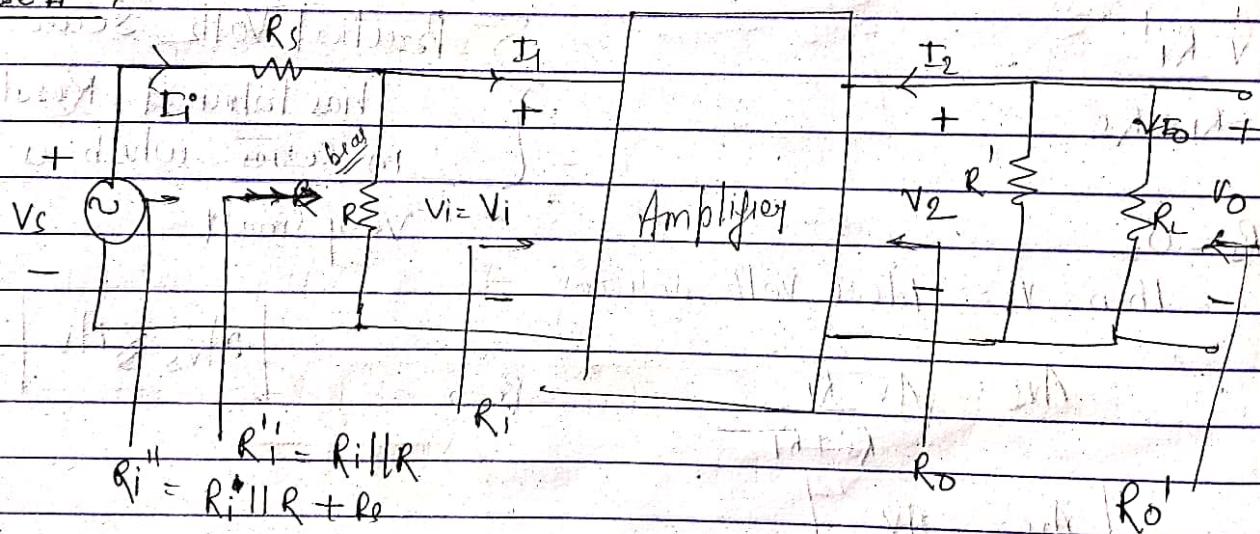

$$R_i'' = R_i' + R_s$$

$$R_o' = R' \parallel R_o + R_s$$

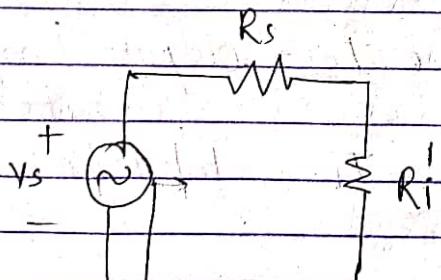

$$R_i'' = R_s + R_i'$$

{ There will be no series resistance in output - 3

Date \_\_\_\_\_  
Page \_\_\_\_\_

Internal Volt gain  $A_v = \frac{V_o}{V_i} = \frac{V_o}{V_i}$

Total Volt gain  $A_s = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s}$

$$A_{vc} = A_v \frac{V_i}{V_s}$$

$$A_{vc} = A_v \frac{R_f}{R_f + R_s}$$


If  $R_s = 0$

$$A_{vs} = A_v = \frac{V_o}{V_i} = \frac{V_o}{V_s}$$

Internal Current gain  $A_i$

Overall Current gain
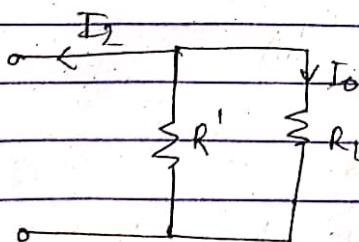
$$A_{ib} = \frac{I_o}{I_i} = \frac{I_o}{I_2} \times \frac{I_2}{I_1} \times \frac{I_1}{I_i}$$




$$I_o = -\frac{I_2 R'}{R' + R_L}$$

$$\frac{I_o}{I_2} = -\frac{R}{R' + R_L}$$

also  $\frac{I_2}{I_1} = A_I$

Date \_\_\_\_\_  
Page \_\_\_\_\_

and

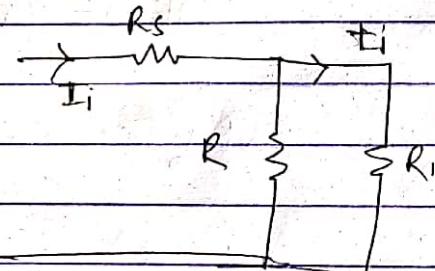

$$I_o = \frac{I_i R}{R + R_i}$$

$$\frac{I_o}{I_i} = \frac{R}{R + R_i}$$

Q2. total (overall) current gain

$$A_{II} = -\left(\frac{R'}{R' + R_i}\right) \times (-A_I) \times \left(\frac{R}{R + R_i}\right)$$

~~A<sub>II</sub>~~

$$A_v [dB] = 20 \log_{10} A_I$$

$$A_I [dB] = 20 \log_{10} A_{II}$$

$$A_p [dB] = 10 \log_{10} A_p$$